

RUHR-UNIVERSITÄT BOCHUM

# Yet Another Size Record for AES: A First-Order SCA Secure AES S-box Based on $GF(2^8)$ Multiplication

SPONSORED BY THE



Federal Ministry Grant. Nr.  
of Education  
and Research 16KIS0666  
SYSKIT\_HW

Cardis 2018, Montpellier

Felix Wegener, Amir Moradi

Ruhr University Bochum, Horst Görtz Institute for IT-Security, Germany

# Problem:

## How to find a small AES S-box implementation (with side-channel protection)?


# AES S-box Implementations

- Naive implementation:




# AES S-box Implementations

- Canright:

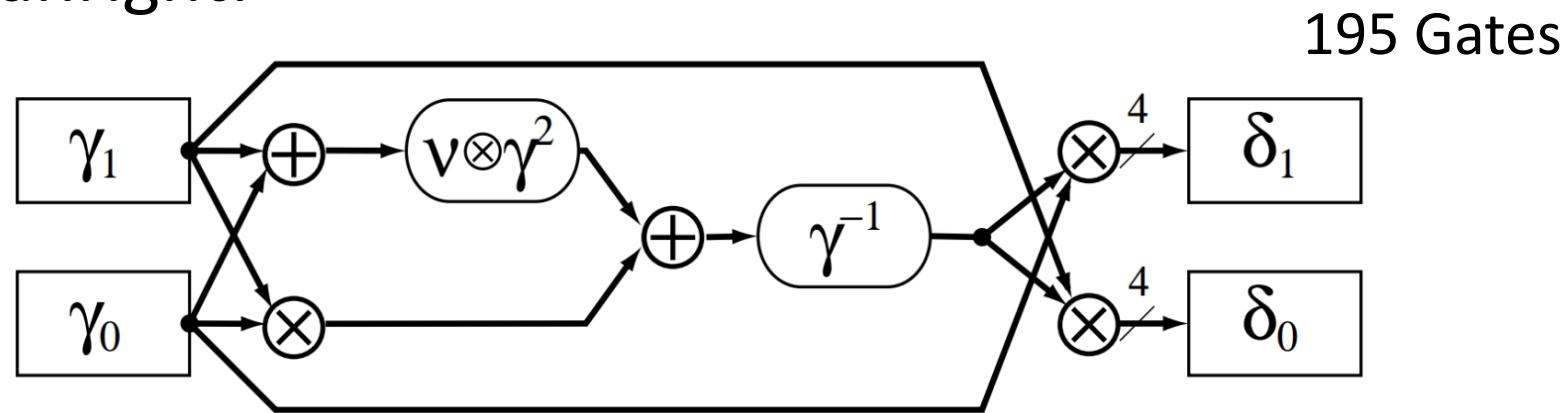

Canright. A Very Compact S-box for AES. CHES 2005


- Boyar, Matthews, Peralta:

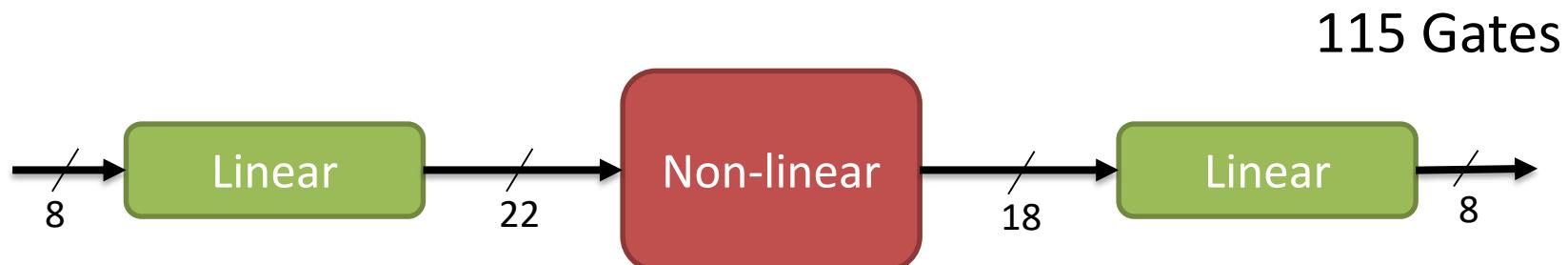


Boyar et al., *Logic Minimization Techniques with Applications to Cryptology*, J. Cryptology 2013

# Issue I: Registers for Bypass Wires

- Canright:

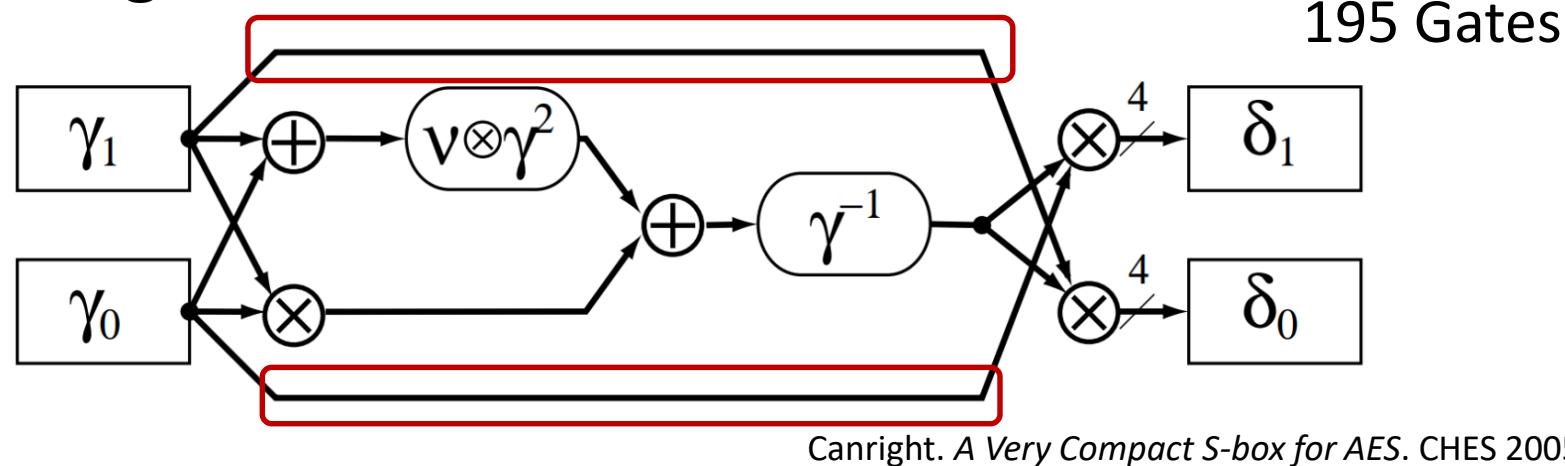


- Boyar, Matthews, Peralta:

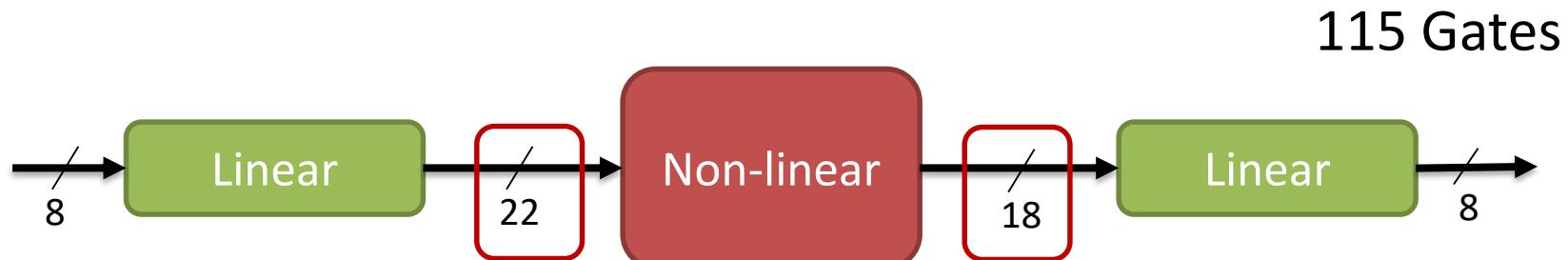


Boyar et al., *Logic Minimization Techniques with Applications to Cryptology*, J. Cryptology 2013

## Issue II: No Serialization Possible

- Canright:

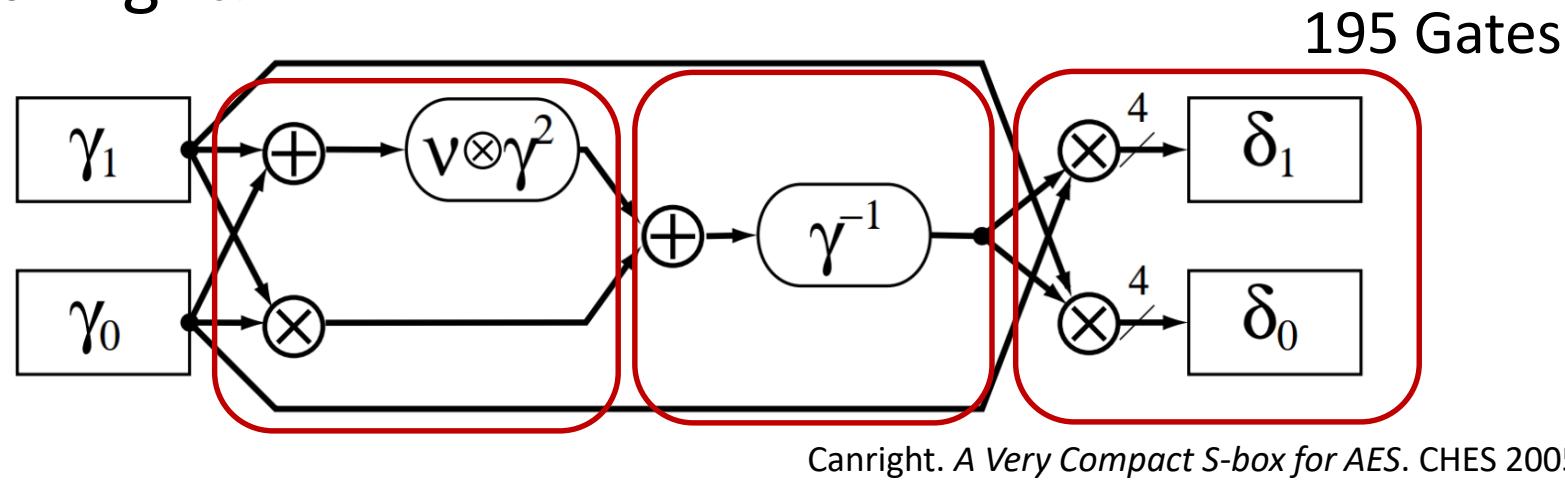


- Boyar, Matthews, Peralta:

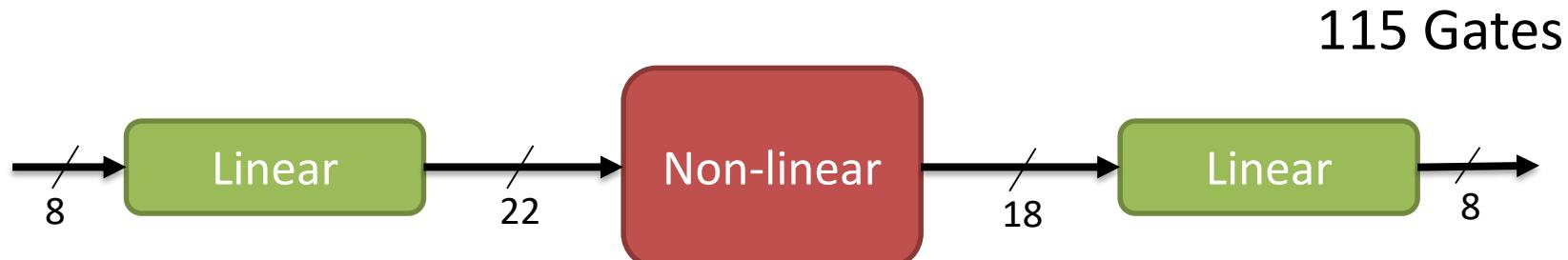

Boyar et al., *Logic Minimization Techniques with Applications to Cryptology*, J. Cryptology 2013

# A Different Structure


- In previous work:

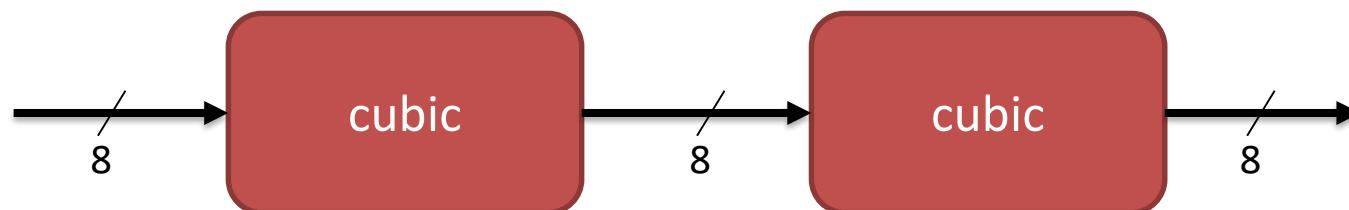

Wegener, Moradi. *A first-order SCA resistant AES without fresh randomness*. COSADE 2018


# A Different Structure: Multiplication-based

- In previous work:

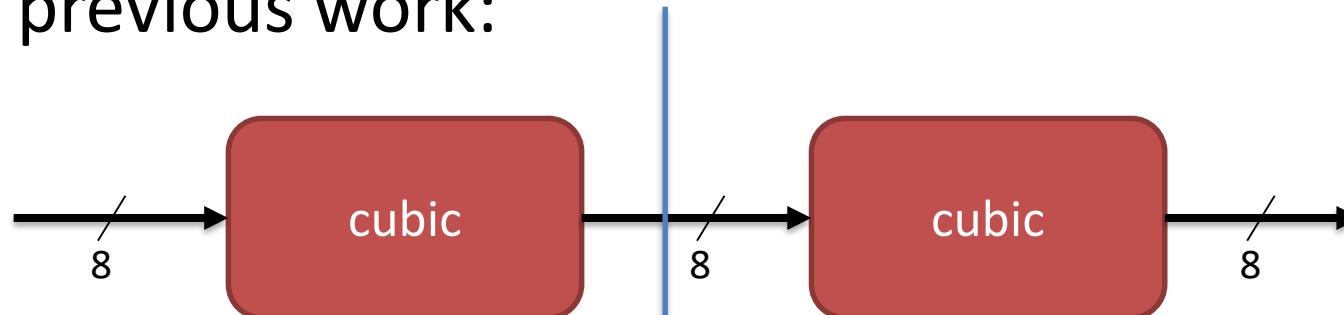

Wegener, Moradi. *A first-order SCA resistant AES without fresh randomness*. COSADE 2018

- This work:

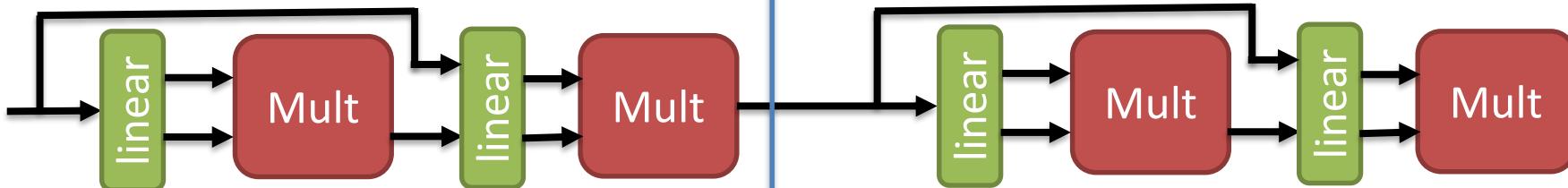

# Decomposition into Multiplications

# Structure of AES S-box

- AES-Sbox ( $x$ ):  $Aff(x^{-1})$
- Inversion in  $GF(2^8)$ :  $x^{-1} = x^{254}$

## Structure of AES S-box

- AES-Sbox ( $x$ ):  $Aff(x^{-1})$
- Inversion in  $GF(2^8)$ :  $x^{-1} = x^{254}$
- How many multiplications are necessary?  
→ Find shortest multiplication chain

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1,$

Cost: 0,

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2,$

Cost: 0, 0,

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2, x^4,$

Cost: 0, 0, 0,

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2, x^4, x^8,$

Cost: 0, 0, 0, 0,

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2, x^4, x^8, x^{12},$

Cost: 0, 0, 0, 0, 1,

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2, x^4, x^8, x^{12}, x^{13}$

Cost: 0, 0, 0, 0, 1, 2

# Multiplication Chain

- Start:  $id = x^1$
- Step:
  - Square a previous element  $\rightarrow$  cost = 0
  - Multiply two previous elements  $\rightarrow$  cost = 1
- Example chain for  $x^{13}$  :

Chain:  $x^1, x^2, x^4, x^8, x^{12}, x^{13}$


Cost: 0, 0, 0, 0, 1, 2

- Lowest cost of chain for  $x^{254}$ : 4

# Multiplication Chain


- $S = x^{254}$
- $L = \log_2(254) = 8$
- What is the “best” way to implement  $x^{254}$  with 4 multiplications?

# Area Reduction Techniques

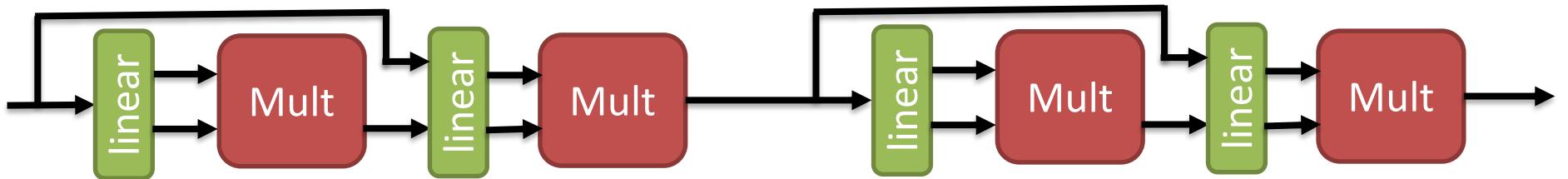


# Area Reduction Techniques

- Limit bypass wires

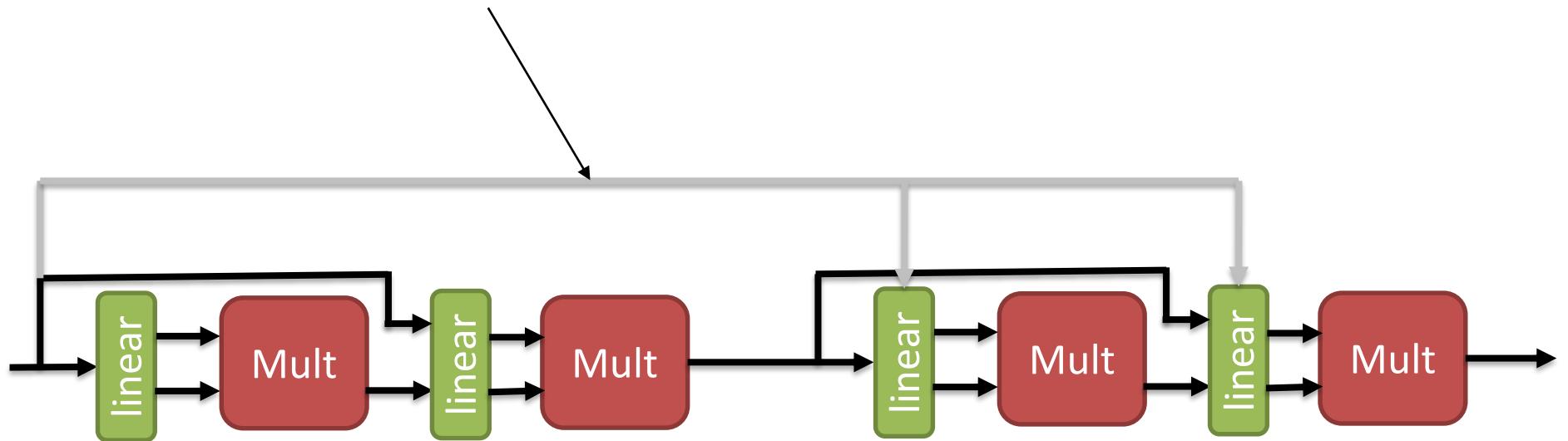

# Area Reduction Techniques


- Limit bypass wires

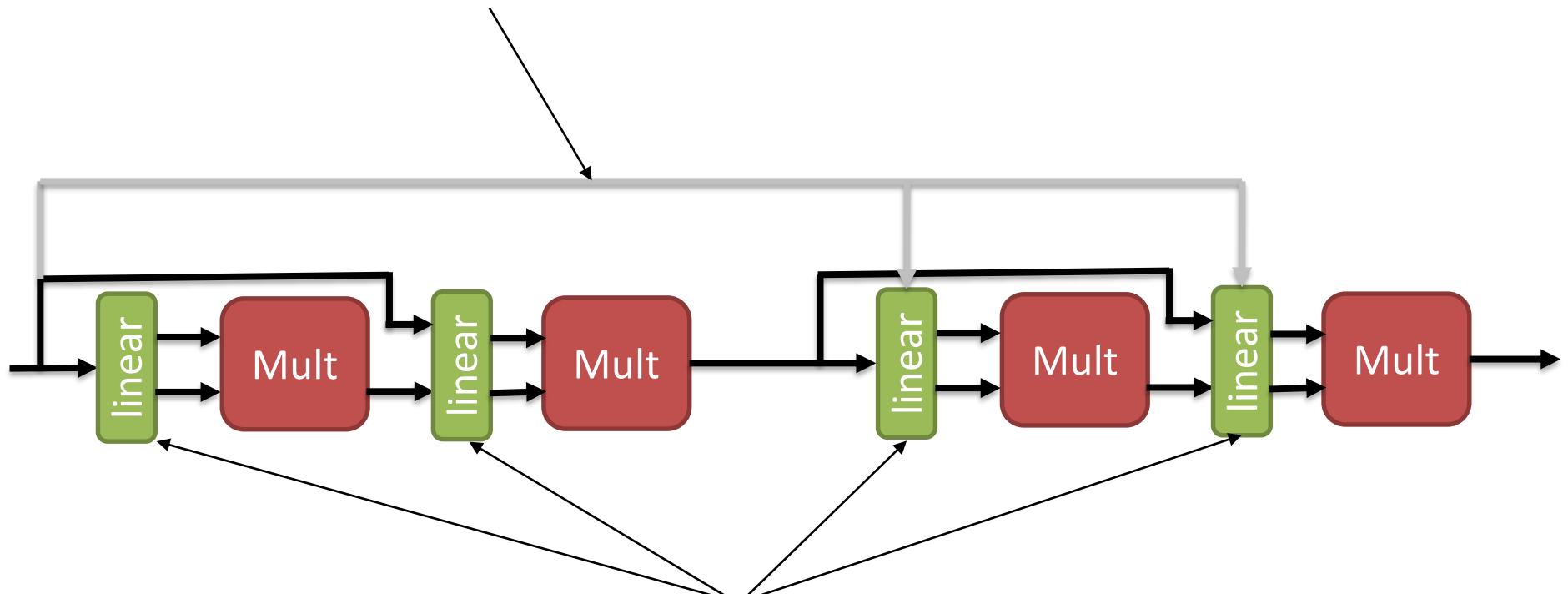

- Minimize linear components

# Area Reduction Techniques


- Limit bypass wires

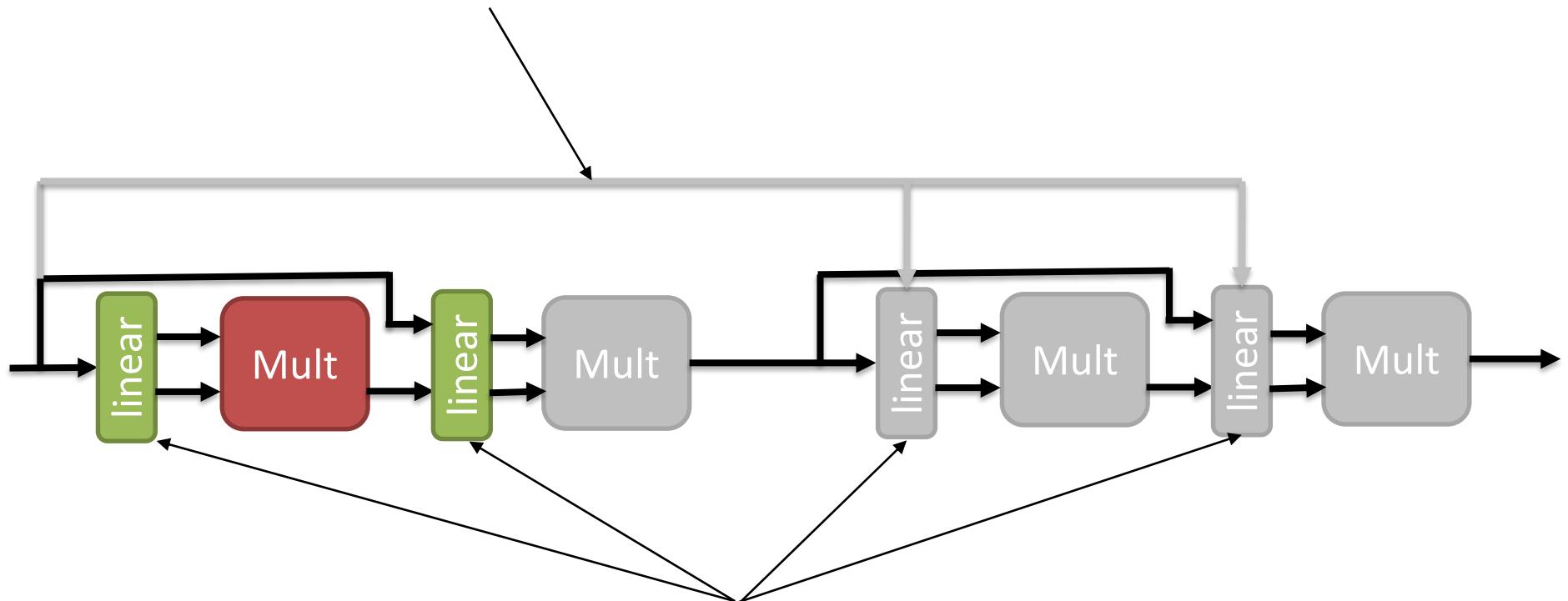

- Minimize linear components
- Serialize: One Multiplier instance


# Our Design: High-Level Structure

- One multiplier instance

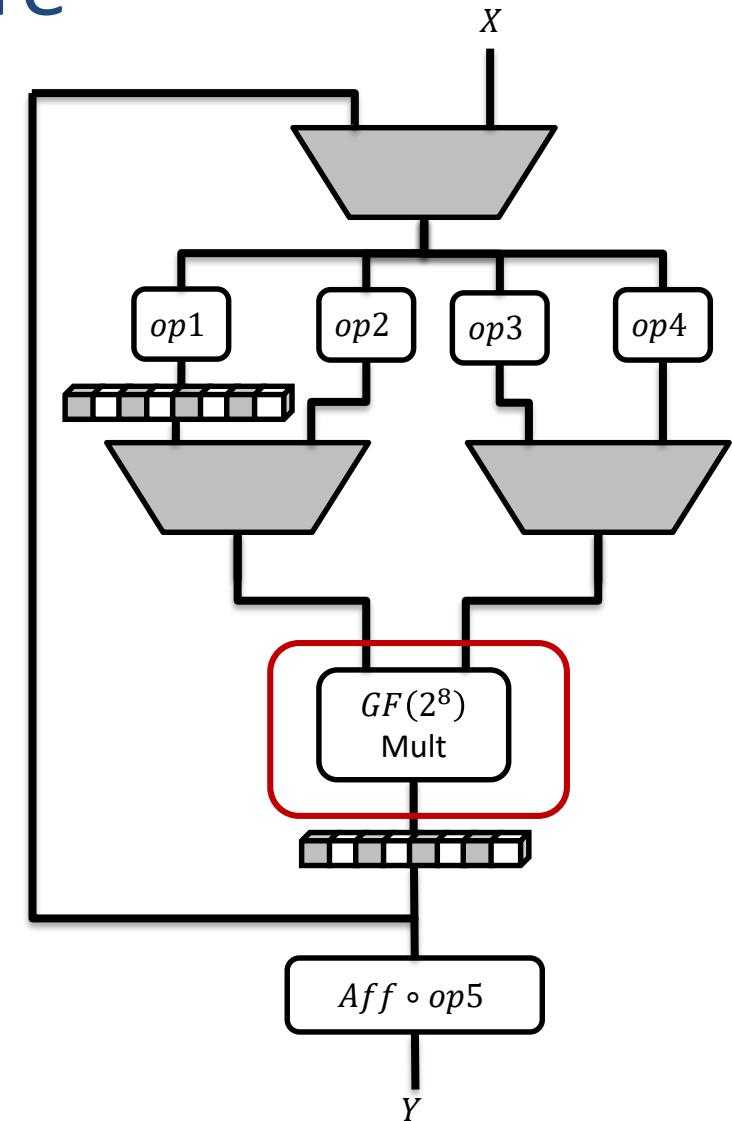

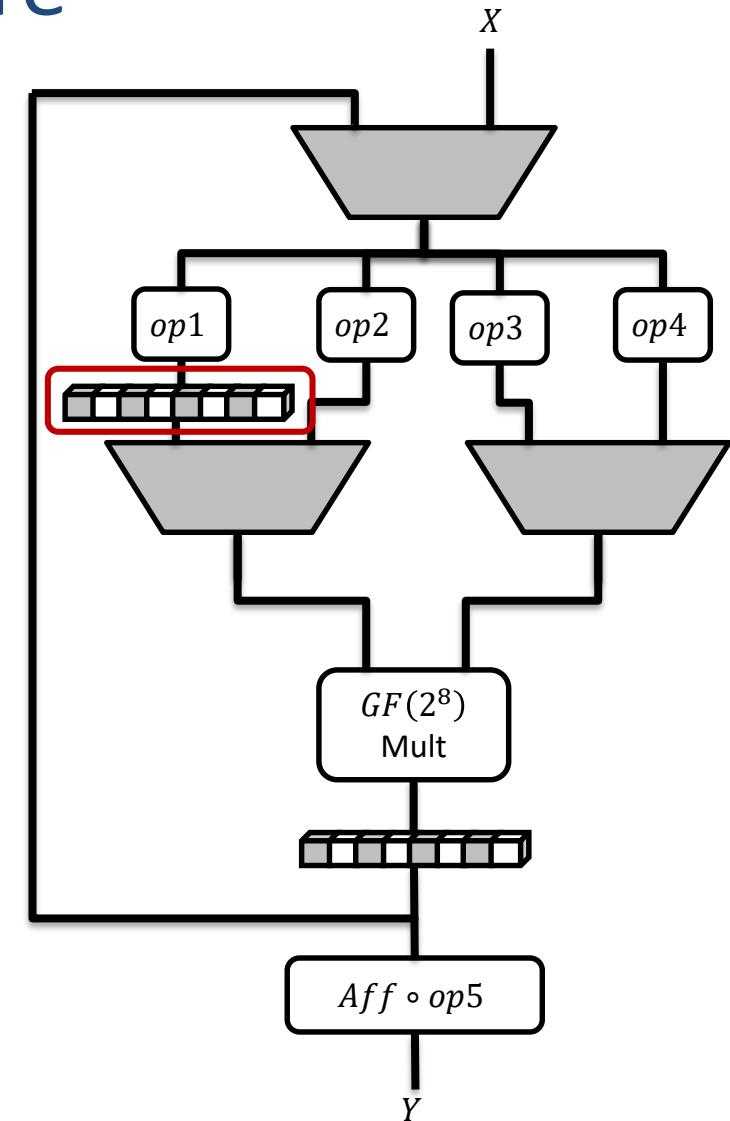
# Our Design: High-Level Structure

- One multiplier instance
- One bypass wire


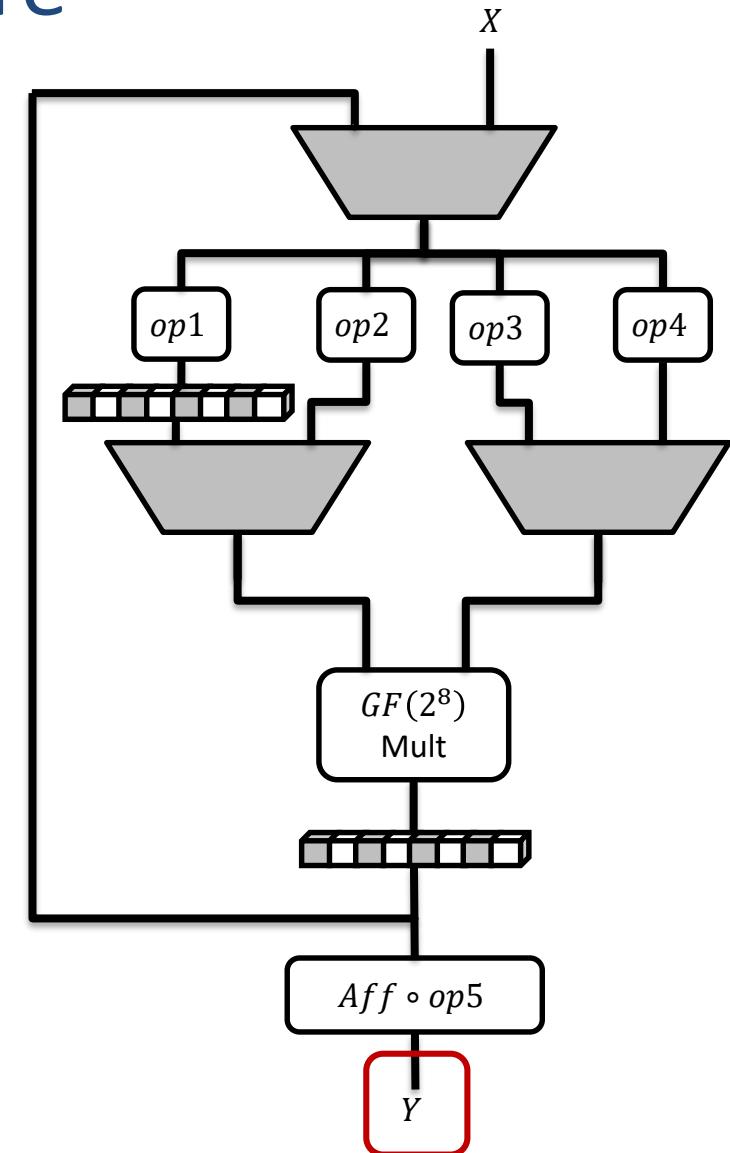
# Our Design: High-Level Structure


- One multiplier instance
- One bypass wire
- $Y = Sbox(X)$  (after 4 iterations)



# Our Design: High-Level Structure

- One multiplier instance
- One bypass wire
- $Y = Sbox(X)$  (after 4 iterations)
- Linear power functions of form

$$op_i = x^{2^k}$$

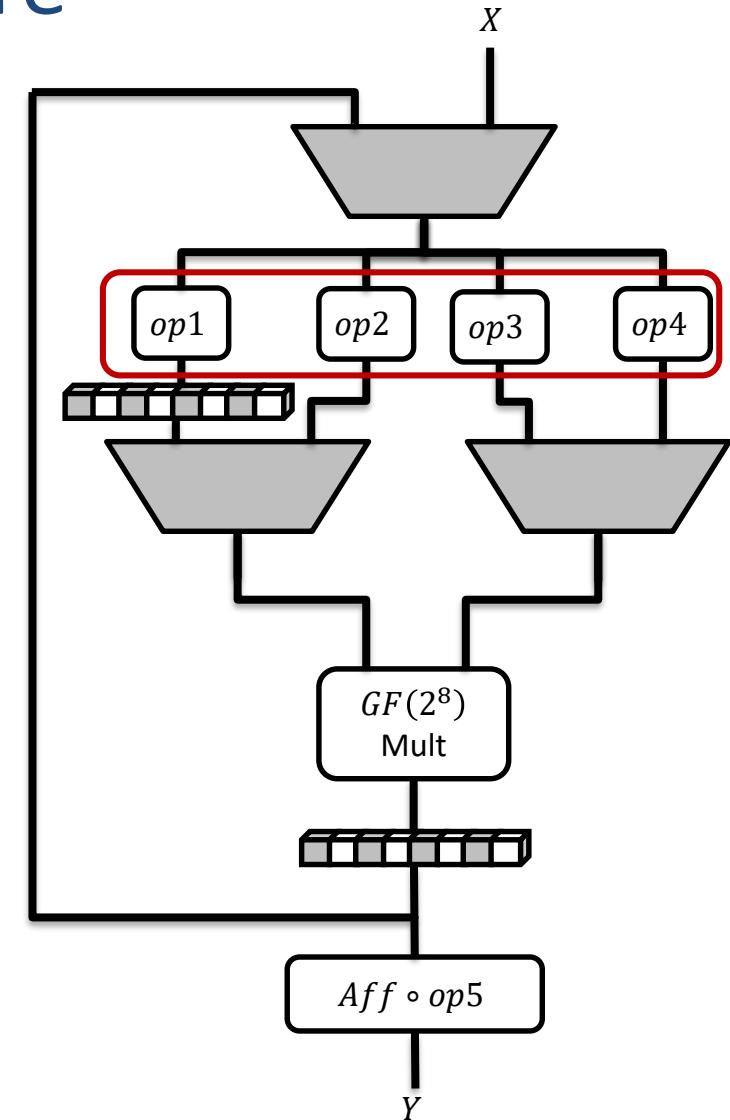


# Our Design: High-Level Structure

- One multiplier instance
- One bypass wire
- $Y = Sbox(X)$  (after 4 iterations)
- Linear power functions of form

$$op_i = x^{2^k}$$

Goal: Minimize total area

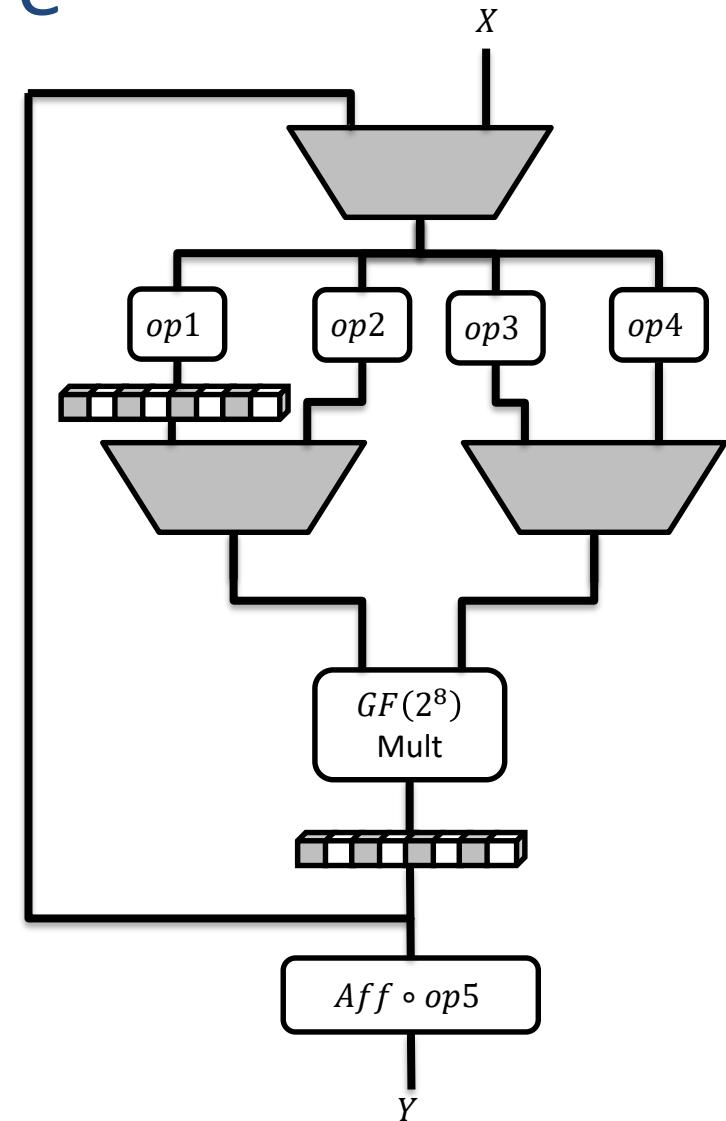

# Area Minimization


Two Steps:

- Determine area of each linear component
- Choose op1, ..., op5 to minimize the total area

UMC 180 nm

Function	Area (GE)	
$x^{128}$	23.7	$x^{128} \parallel x^{16}$ 52.3
$x^{16}$	33.3	$x^{128} \parallel x^2$ 41.3
$x^2$	22.7	$x^{128} \parallel x^{32}$ 49.0
$x^{32}$	33.3	$x^{128} \parallel x^4$ 50.7
$x^4$	31.7	$x^{128} \parallel x^{64}$ 43.7
$x^{64}$	29.7	$x^{128} \parallel x^8$ 47.0
$x^8$	32.0	$x^{16} \parallel x^2$ 44.7
$\text{Aff} \circ x^1$	41.7	$x^{16} \parallel x^4$ 54.3
$\text{Aff} \circ x^{128}$	40.7	$x^{16} \parallel x^8$ 54.3
$\text{Aff} \circ x^{16}$	36.3	$x^{32} \parallel x^{16}$ 49.7
$\text{Aff} \circ x^2$	40.3	$x^{32} \parallel x^2$ 45.0
$\text{Aff} \circ x^{32}$	36.7	$x^{32} \parallel x^4$ 52.3
$\text{Aff} \circ x^4$	36.3	$x^{32} \parallel x^8$ 53.0
$\text{Aff} \circ x^{64}$	29.7	$x^4 \parallel x^2$ 45.7
$\text{Aff} \circ x^8$	34.0	$x^{64} \parallel x^{16}$ 53.7
		$x^{64} \parallel x^2$ 48.3
		$x^{64} \parallel x^{32}$ 53.0
		$x^{64} \parallel x^4$ 53.7
		$x^{64} \parallel x^8$ 51.7
		$x^8 \parallel x^2$ 44.0
		$x^8 \parallel x^4$ 52.0


# Area Minimal Choice

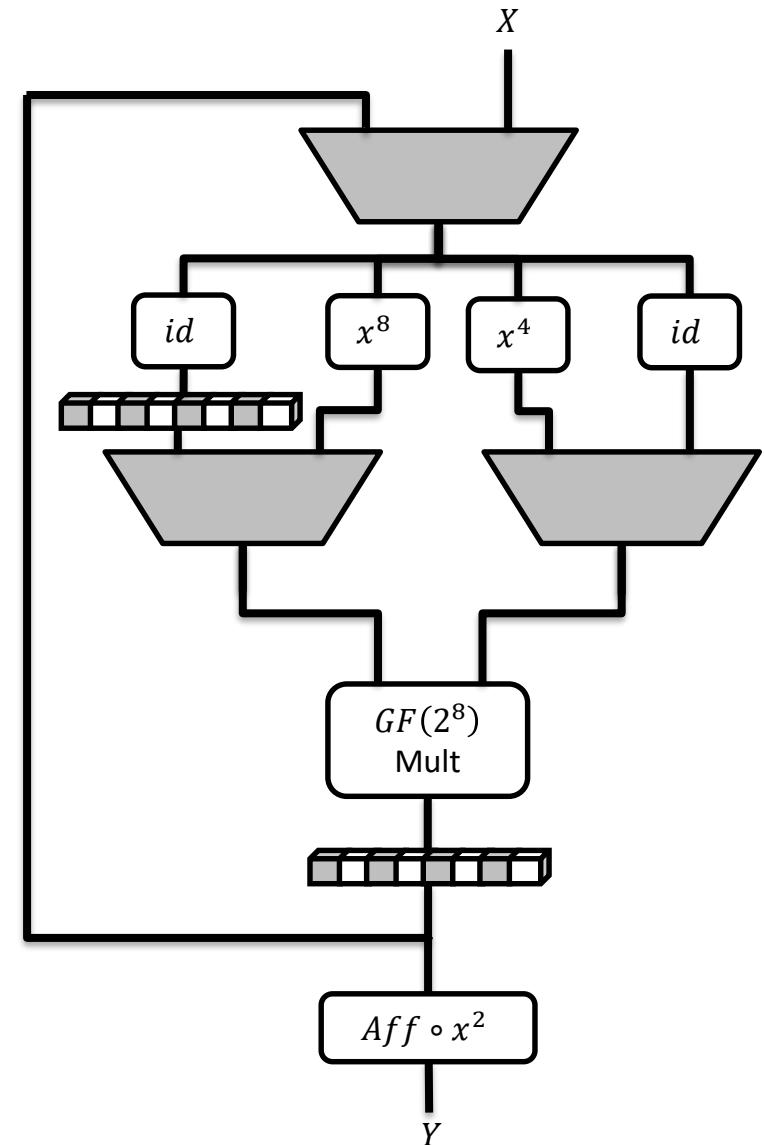

# Area Minimal Choice

- Iteration 1:

$$x^{12} = \text{Mult}(x^8, x^4)$$

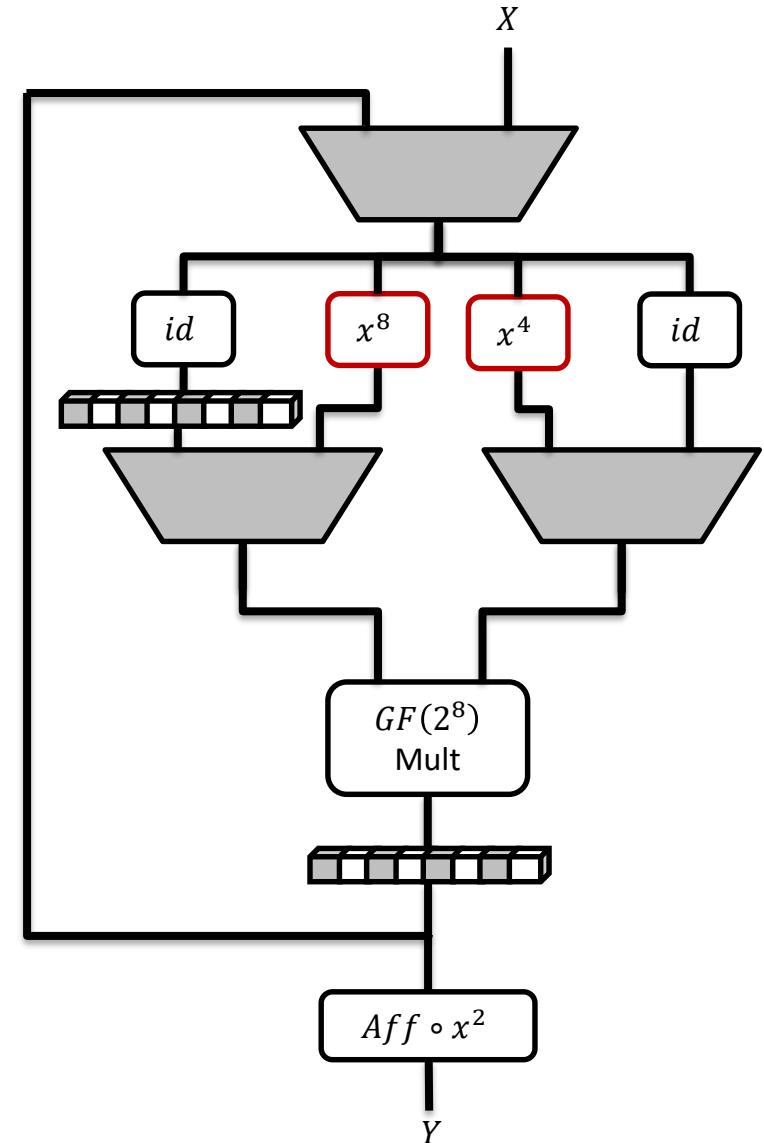


# Area Minimal Choice

- Iteration 1:

$$x^{12} = \text{Mult}(x^8, x^4)$$

- Iteration 2:
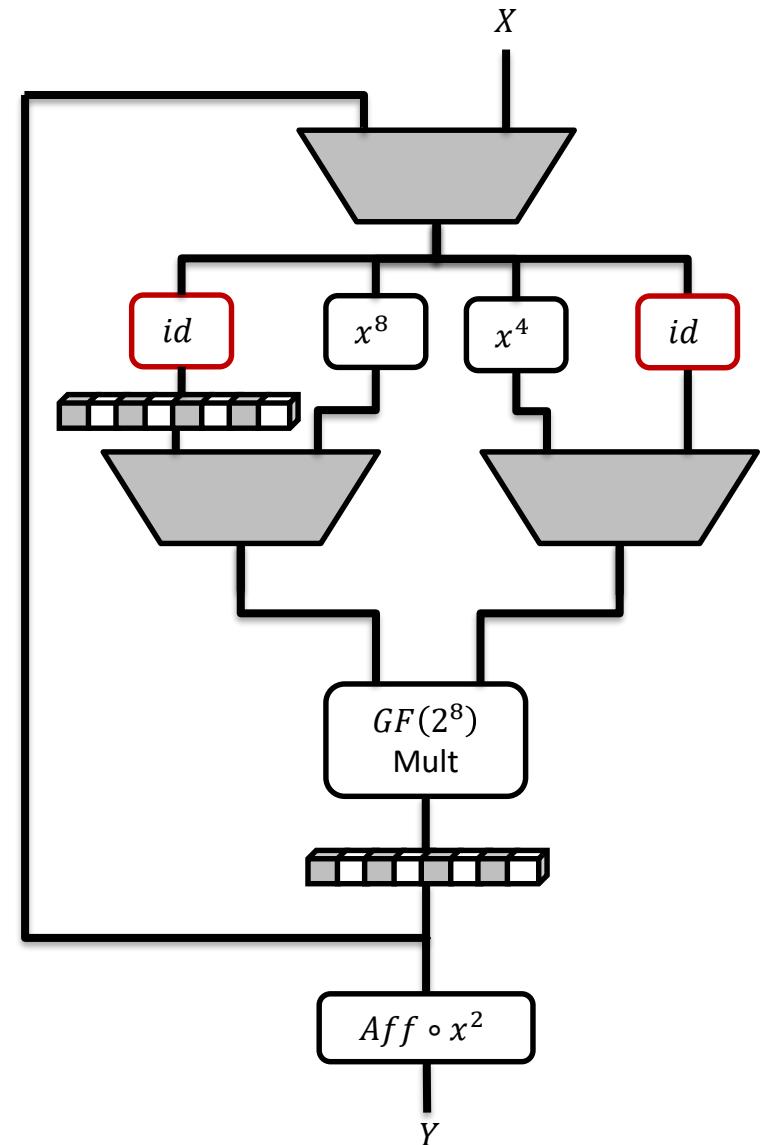
$$x^{13} = \text{Mult}(x^1, x^{12}) =: z$$



# Area Minimal Choice

- Iteration 1:


$$x^{12} = \text{Mult}(x^8, x^4)$$

- Iteration 2:

$$x^{13} = \text{Mult}(x^1, x^{12}) =: z$$

- Iteration 3:

$$z^{12} = \text{Mult}(z^8, z^4)$$

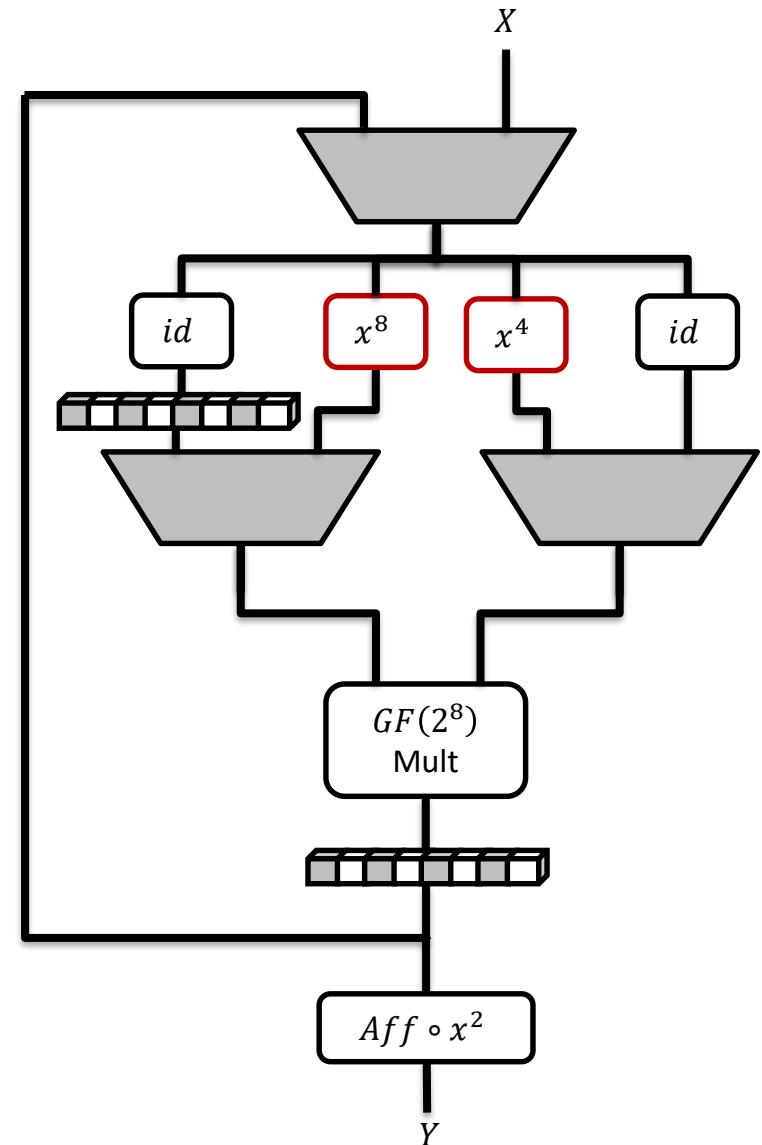

# Area Minimal Choice

- Iteration 1:

$$x^{12} = \text{Mult}(x^8, x^4)$$

- Iteration 2:


$$x^{13} = \text{Mult}(x^1, x^{12}) =: z$$

- Iteration 3:

$$z^{12} = \text{Mult}(z^8, z^4)$$

- Iteration 4:

$$z^{49} = \text{Mult}(z^1, z^{48})$$

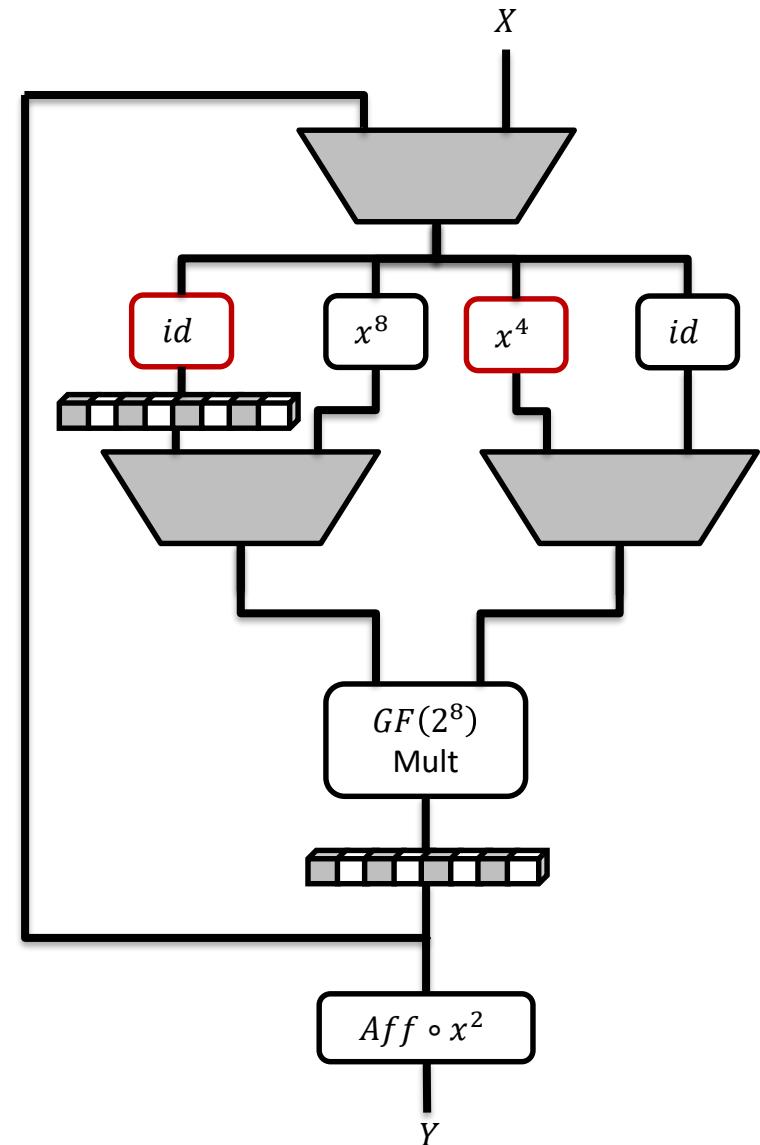

# Area Minimal Choice

- Iteration 1:

$$x^{12} = \text{Mult}(x^8, x^4)$$

- Iteration 2:

$$x^{13} = \text{Mult}(x^1, x^{12}) =: z$$

- Iteration 3:


$$z^{12} = \text{Mult}(z^8, z^4)$$

- Iteration 4:

$$z^{49} = \text{Mult}(z^1, z^{48})$$

- Output:

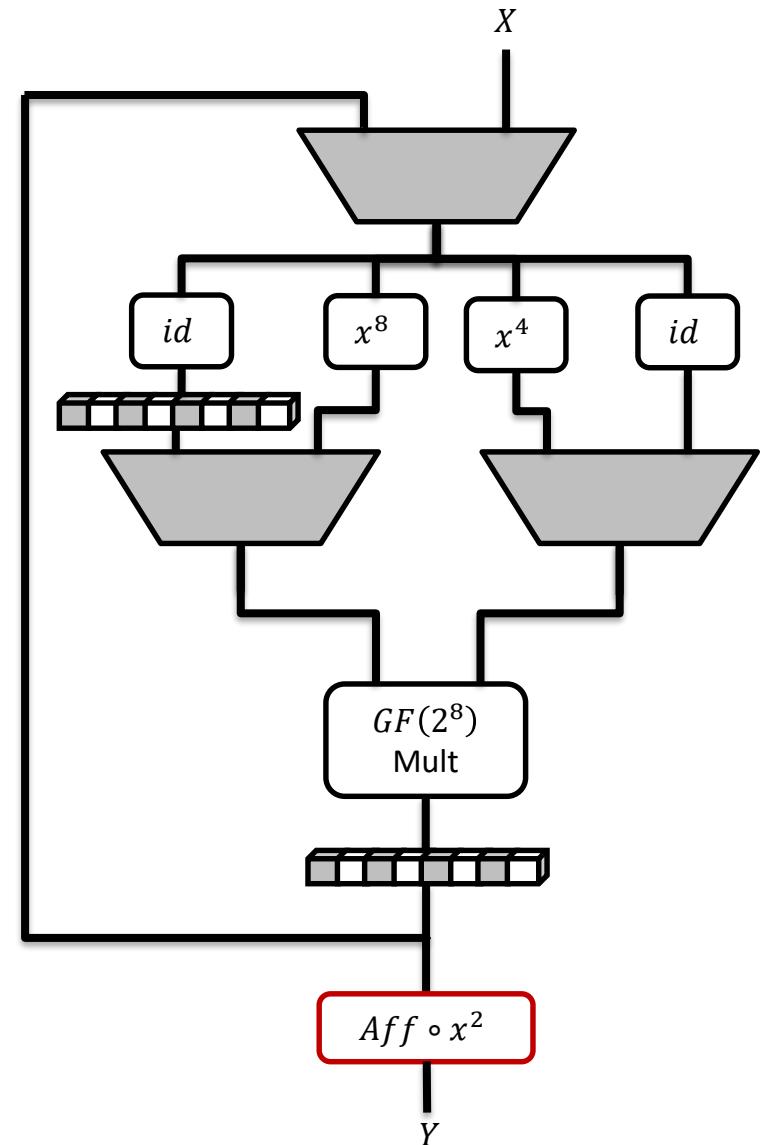
$$Y = \text{Aff}(x^{13 \cdot 49 \cdot 2}) = \text{Aff}(x^{254})$$



# Achieving SCA Security

# Domain-oriented Masking


First-order DOM-independent multiplier:

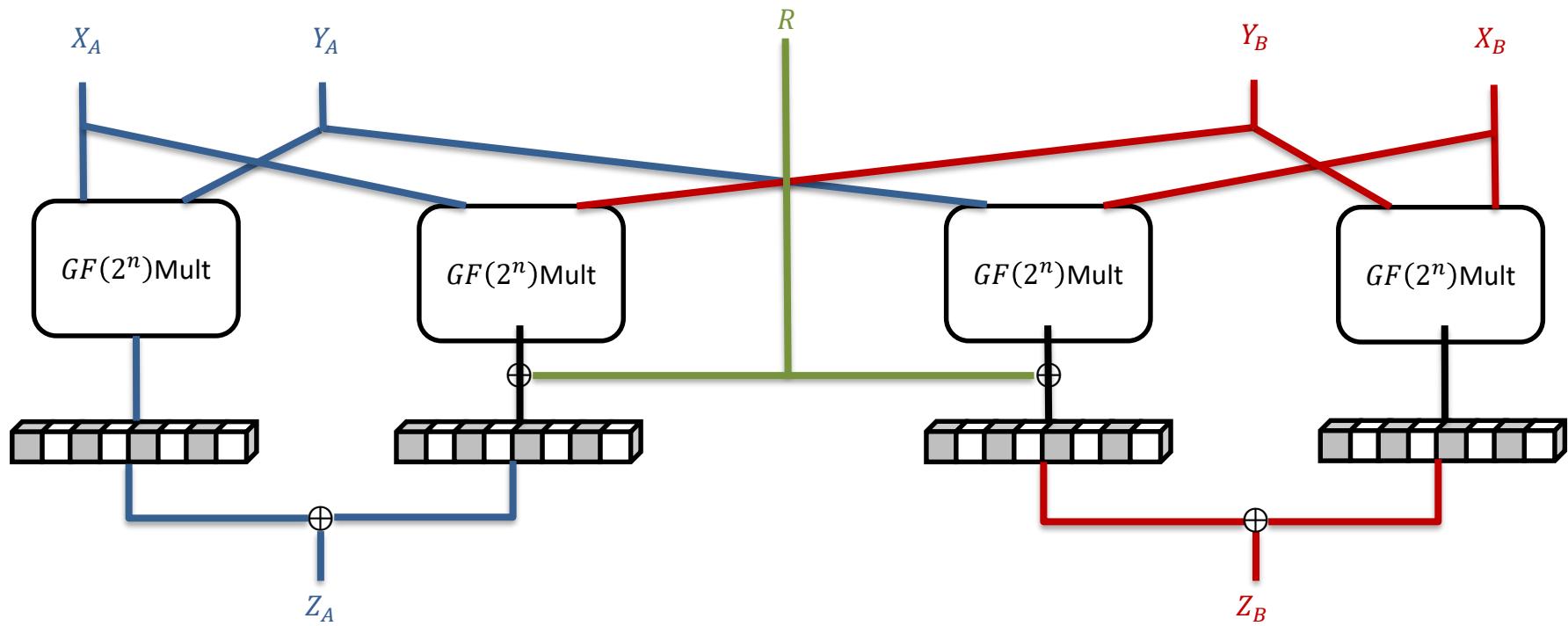

Groß et al. *Domain-Oriented Masking: Compact Masked Hardware Implementations with Arbitrary Protection Order*, CCS 2016


# Domain-oriented Masking

First-order DOM-independent multiplier:

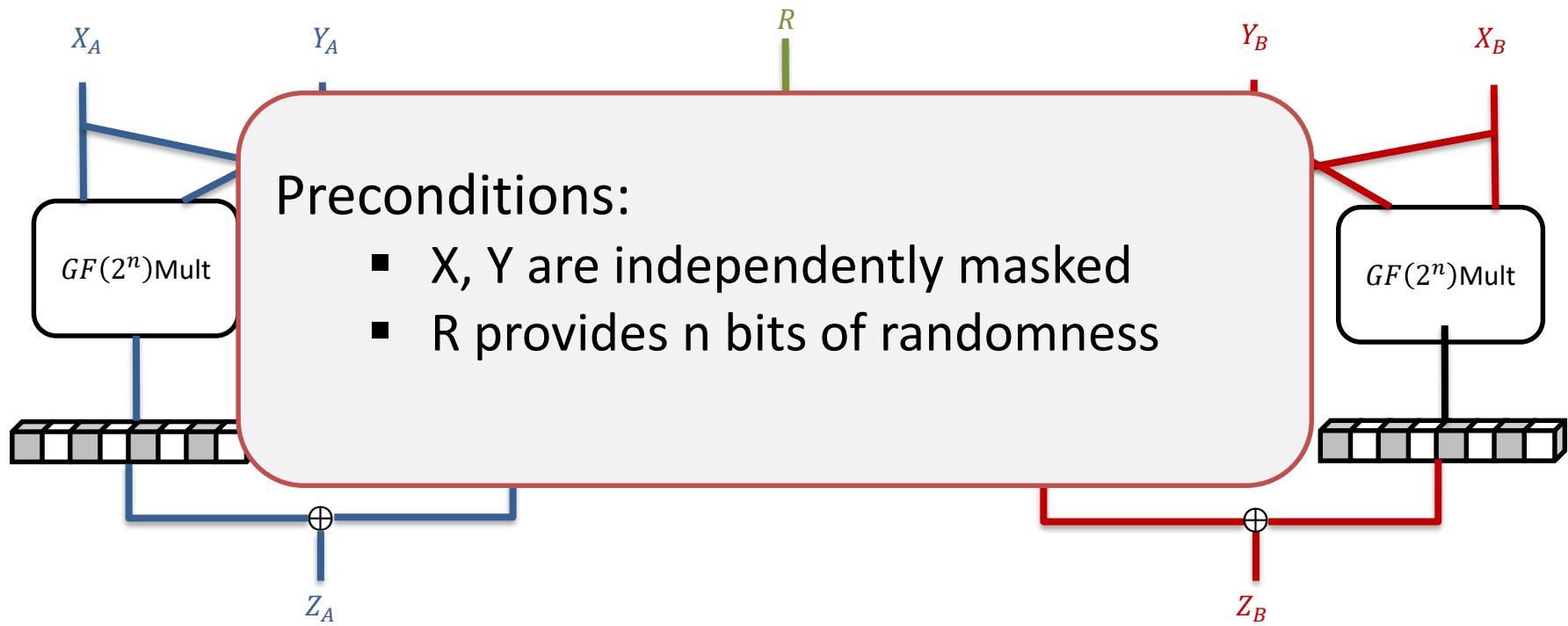


Groß et al. *Domain-Oriented Masking: Compact Masked Hardware Implementations with Arbitrary Protection Order*, CCS 2016


# First-order Secure Design (Generic)

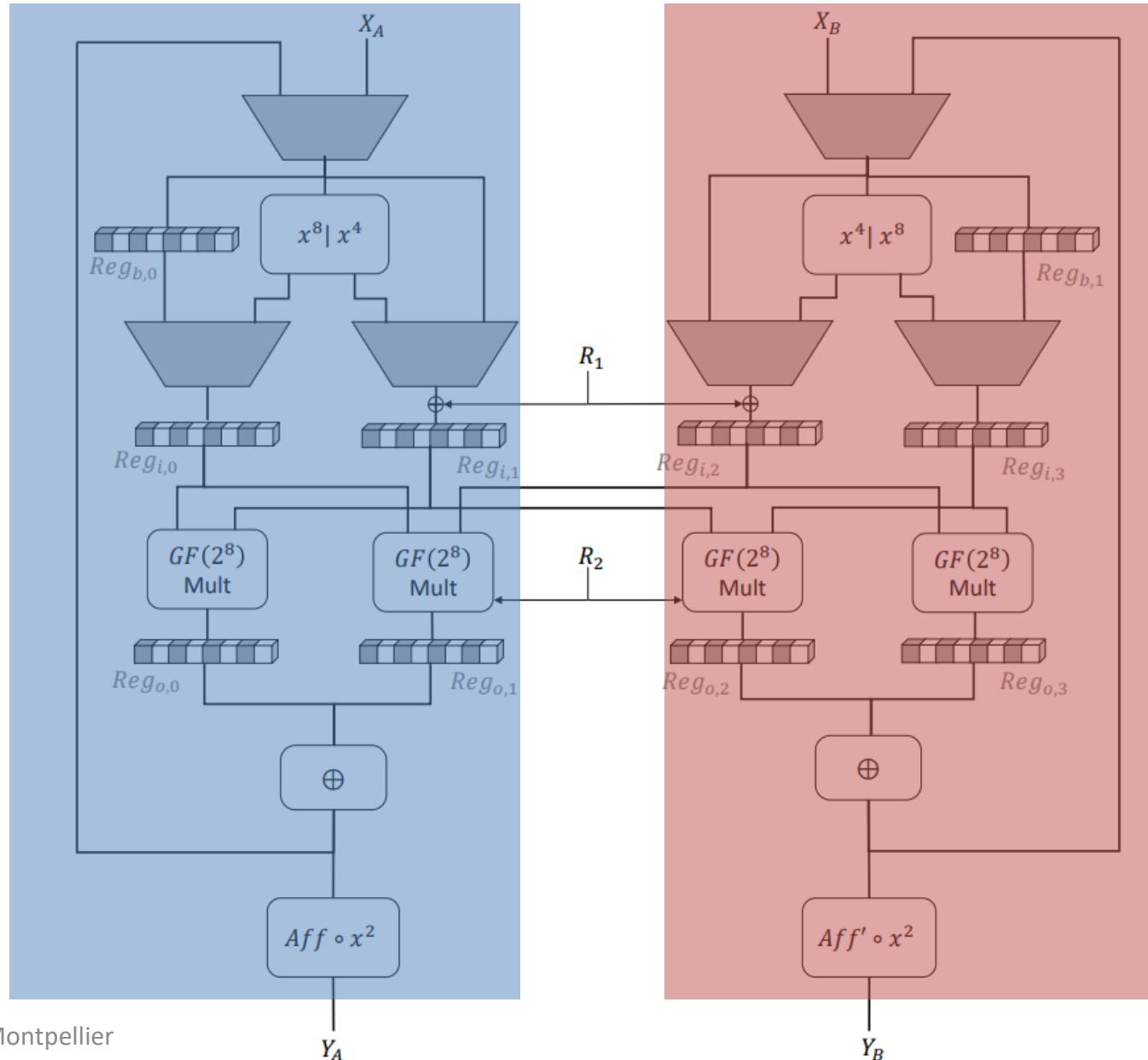

# First-order Secure Design (Generic)

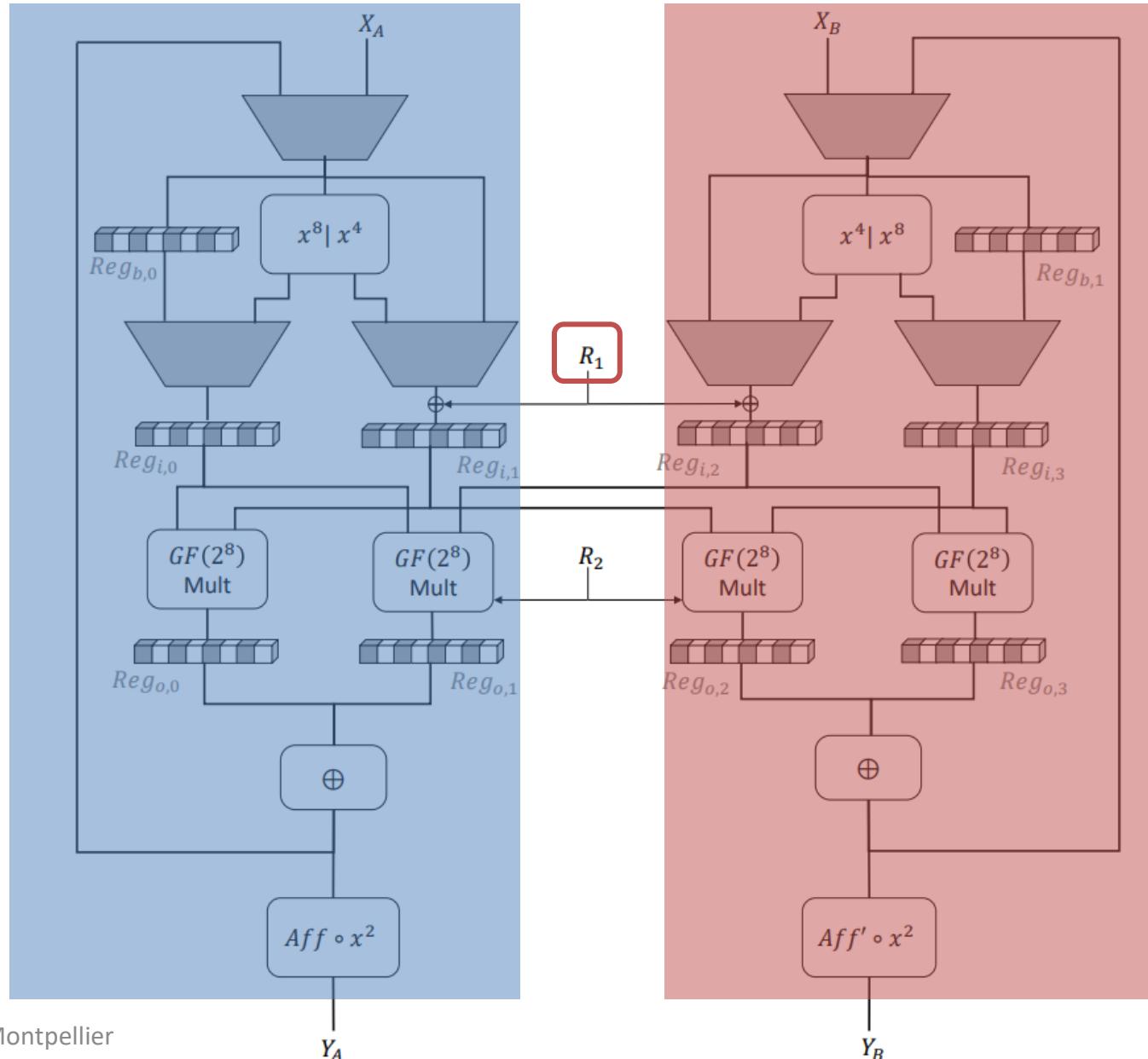


# First-order Secure Design (Generic)

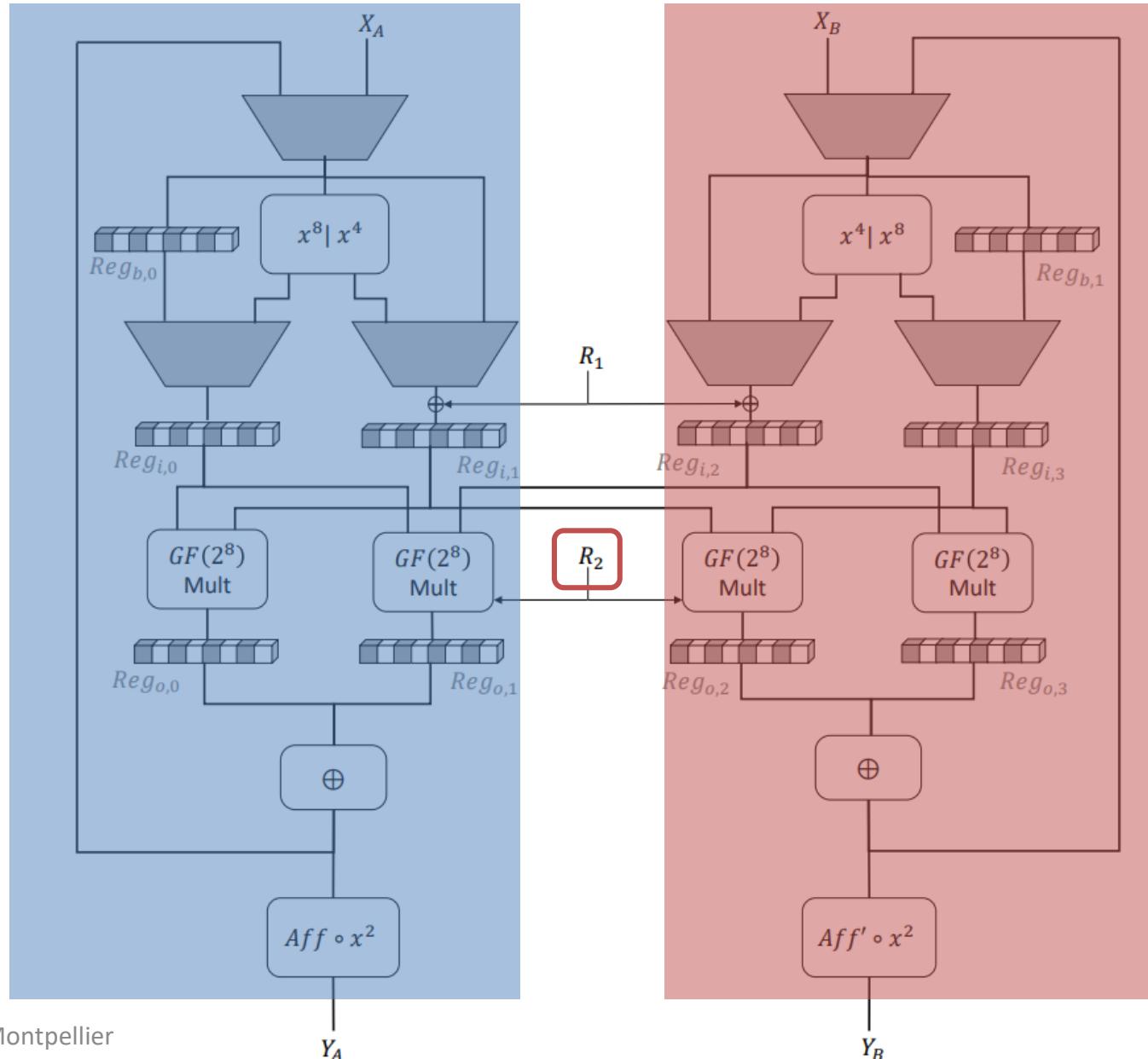


# Design I: Fully-Parallel Multiplier
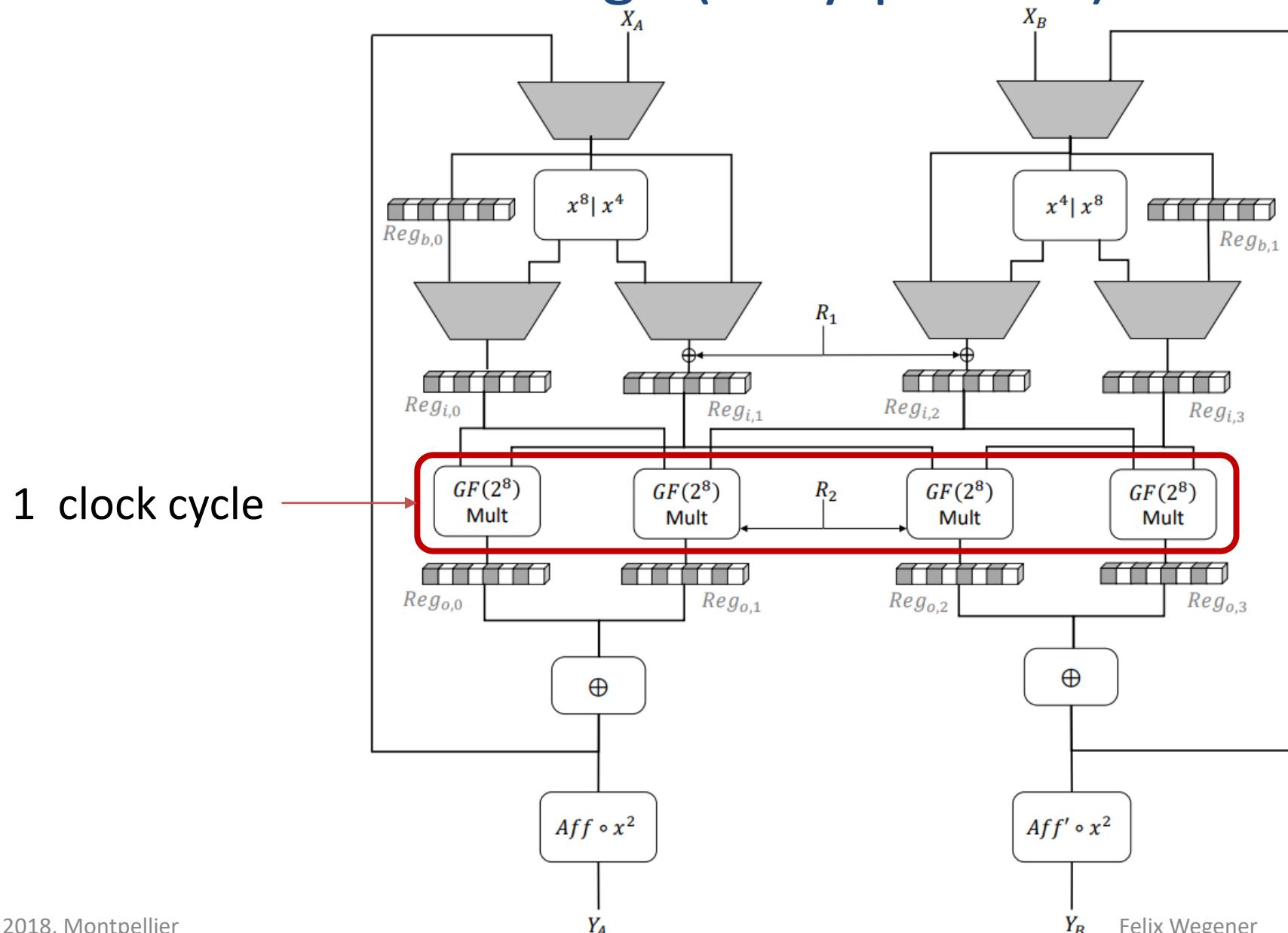
# First-order Secure Design (Fully-parallel)


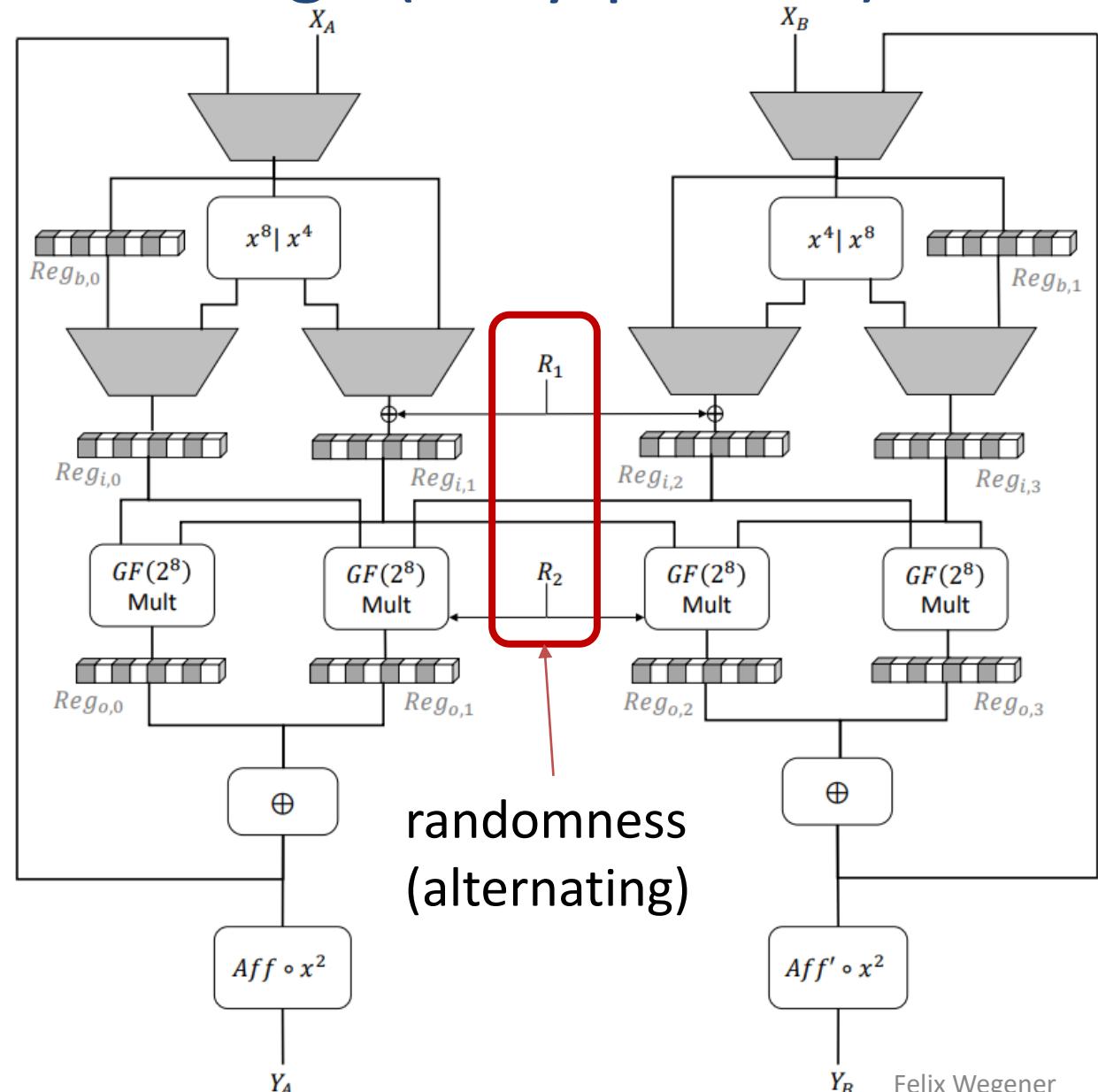
# First-order Secure Design (Fully-parallel)




# First-order Secure Design (Fully-parallel)

Latency:  
8 cycles


Randomness:  
8 bits / cyc.

Area:  
2321 GE

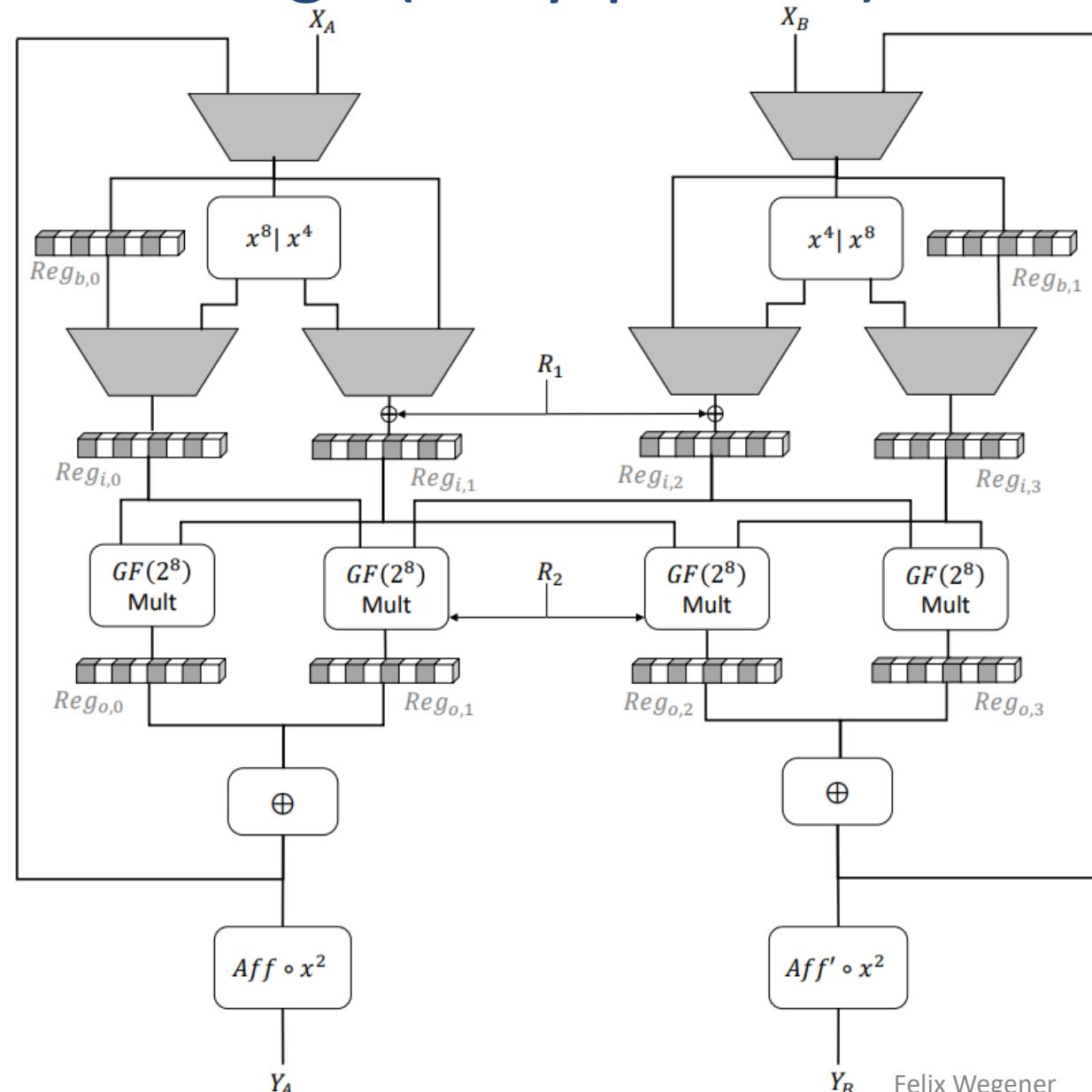


# Design II: Serial-Parallel Multiplier
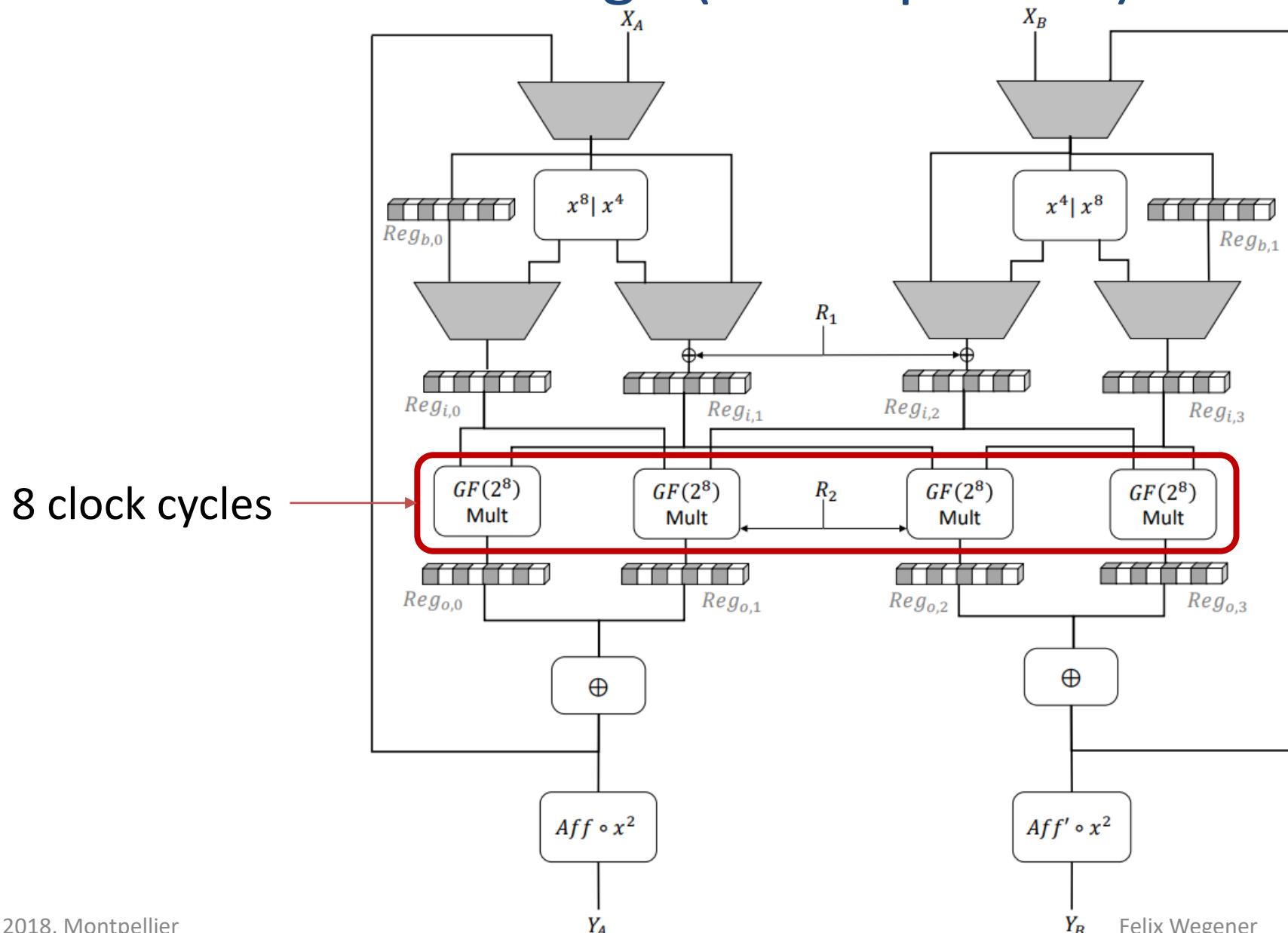
# First-order Secure Design (Serial-parallel)




# First-order Secure Design (Serial-parallel)

Restoring  
independence

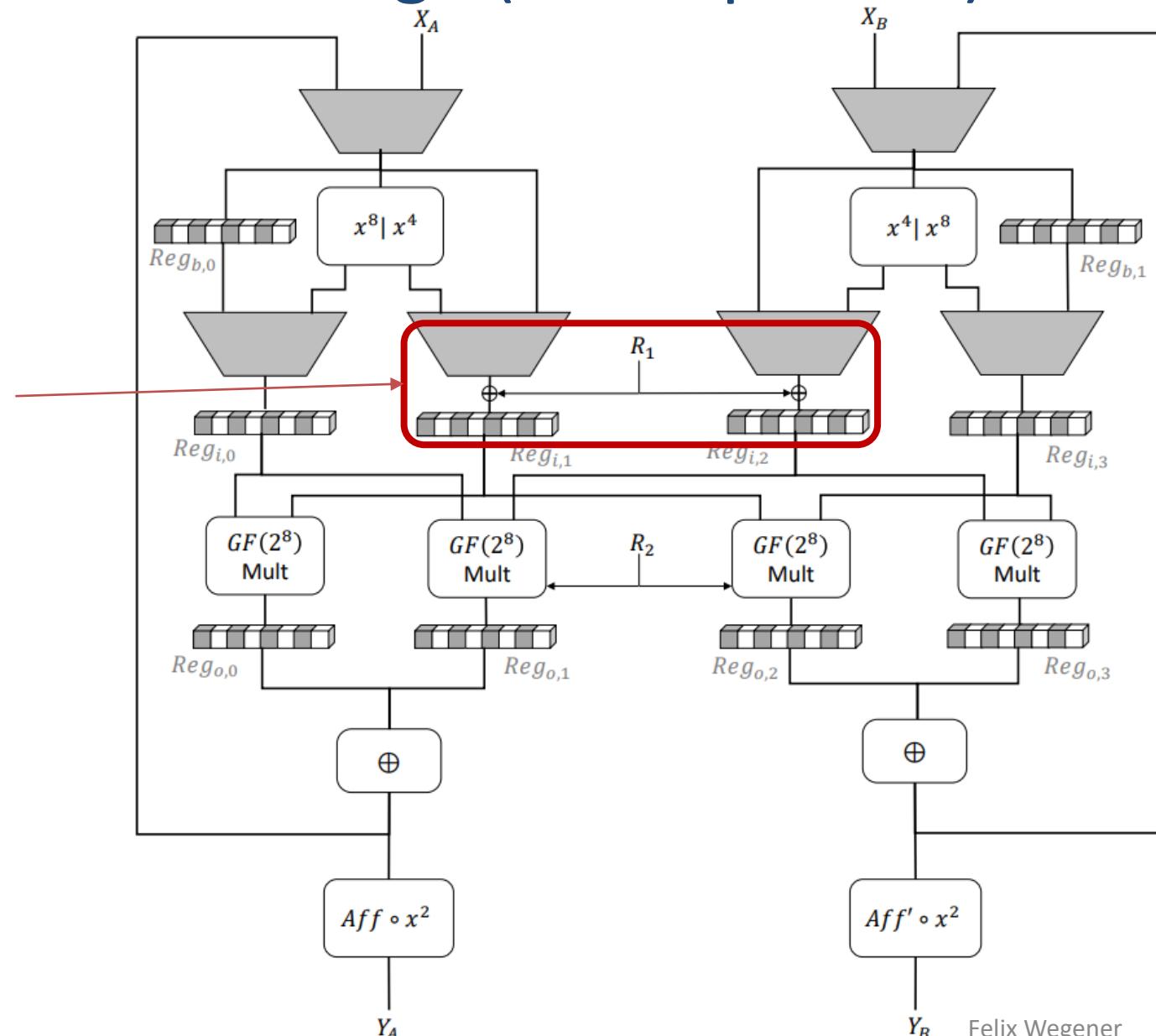

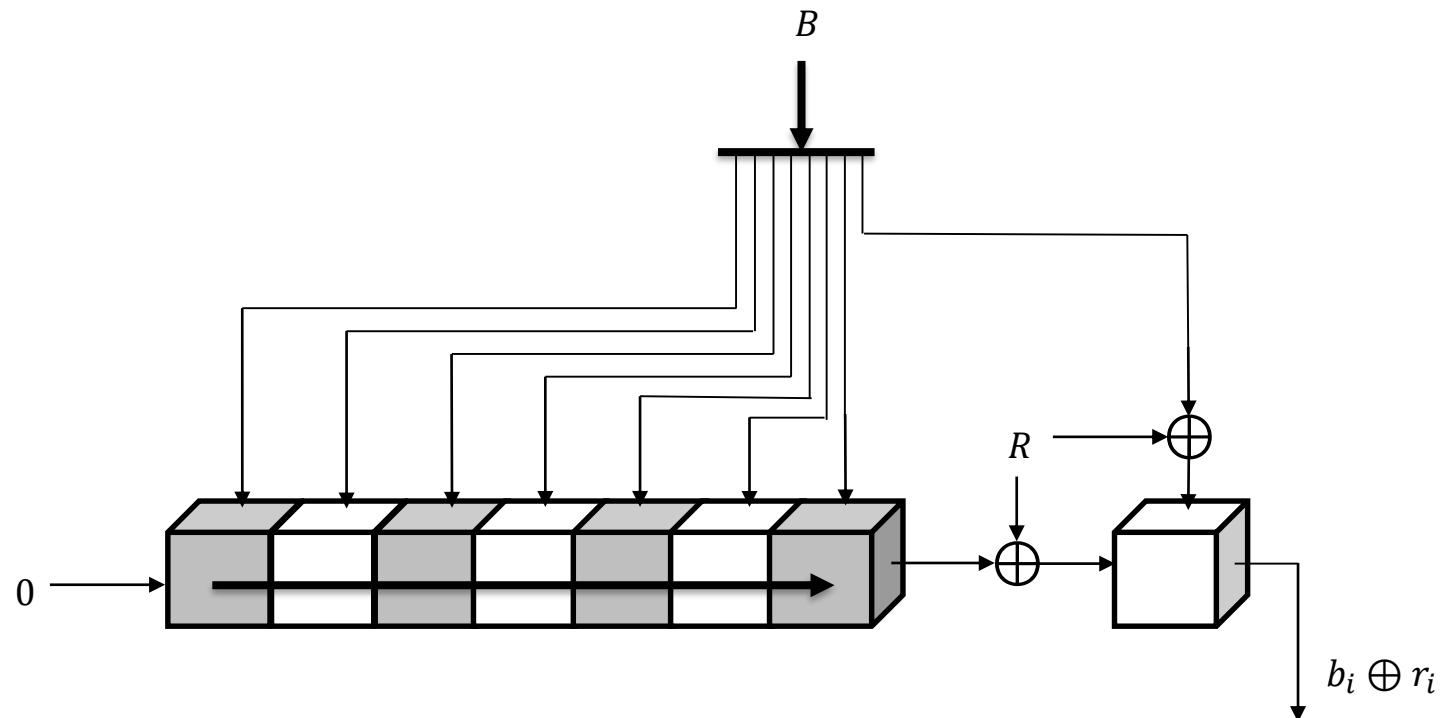
# Restoring Independence

- Goal: 1 bit of randomness / cycle
  - Different path for MSB
  - Re-masked value from Register




# First-order Secure Design (Serial-parallel)

Cross-domain  
remasking

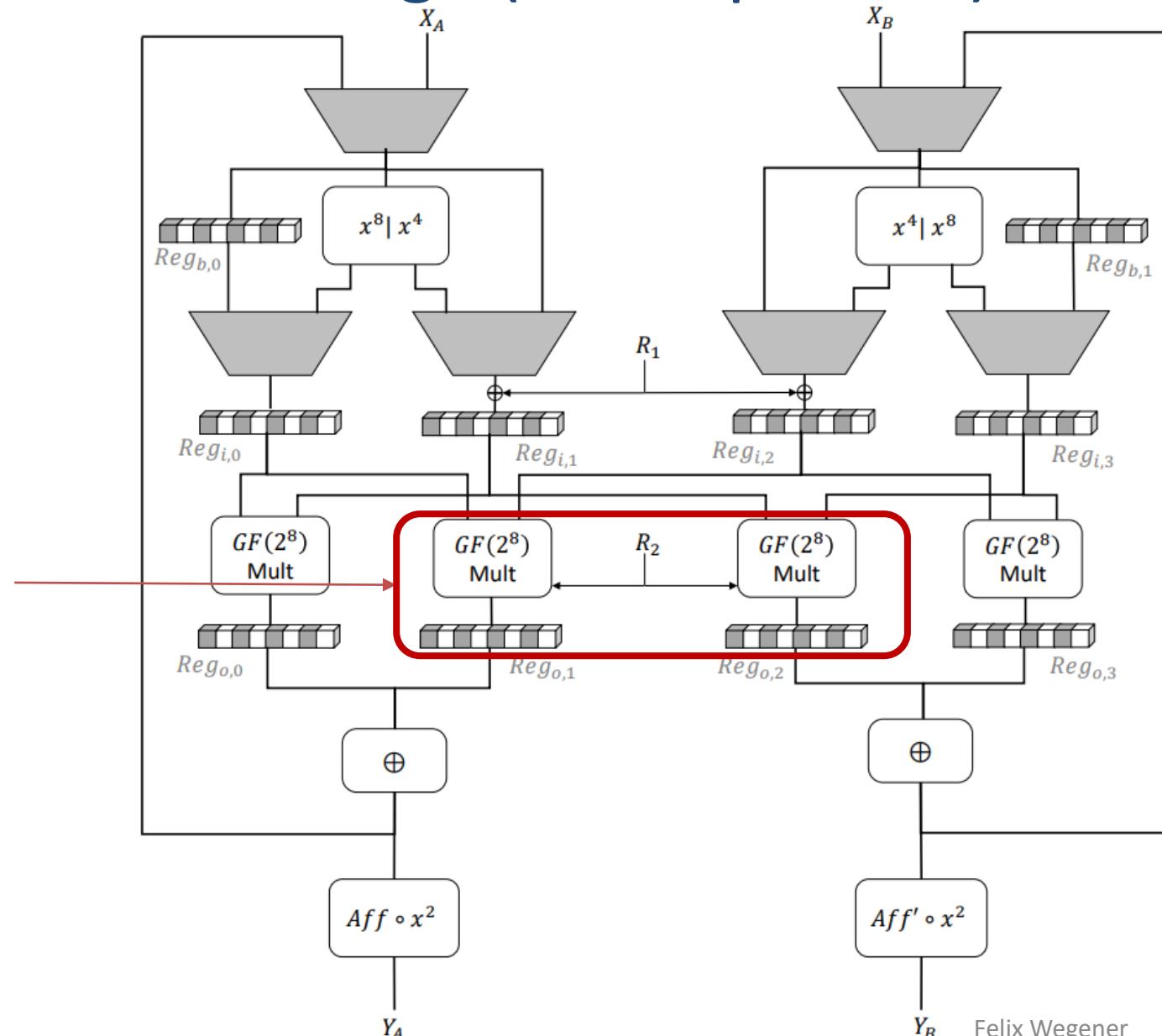

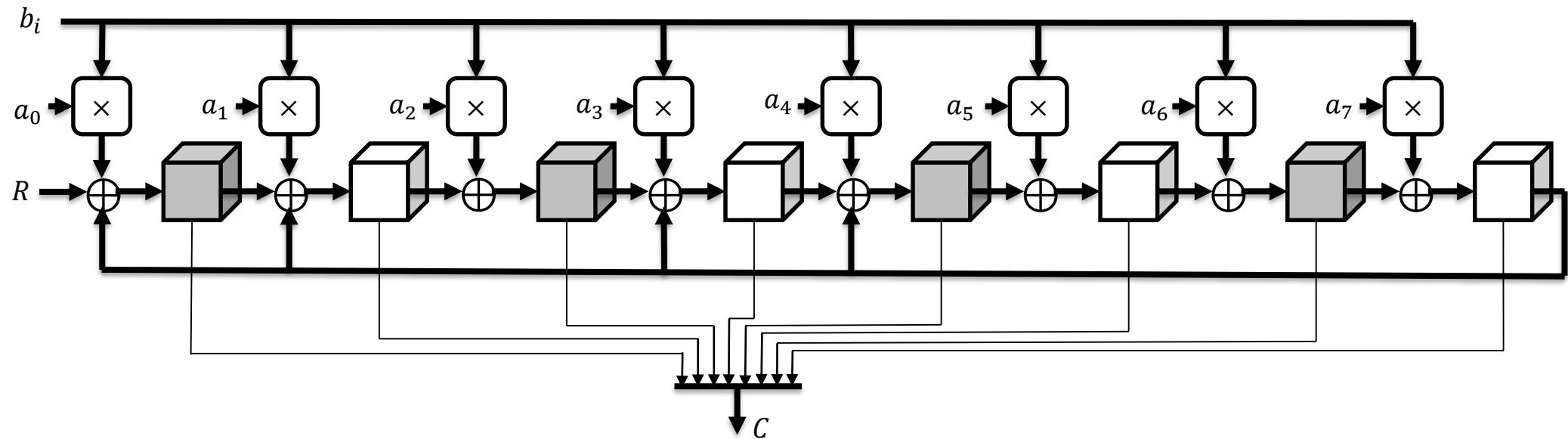
# Serial-Parallel Multiplier

- Inputs:
  - $a$ : 8 bits parallel
  - $b$ : 1 bit serial


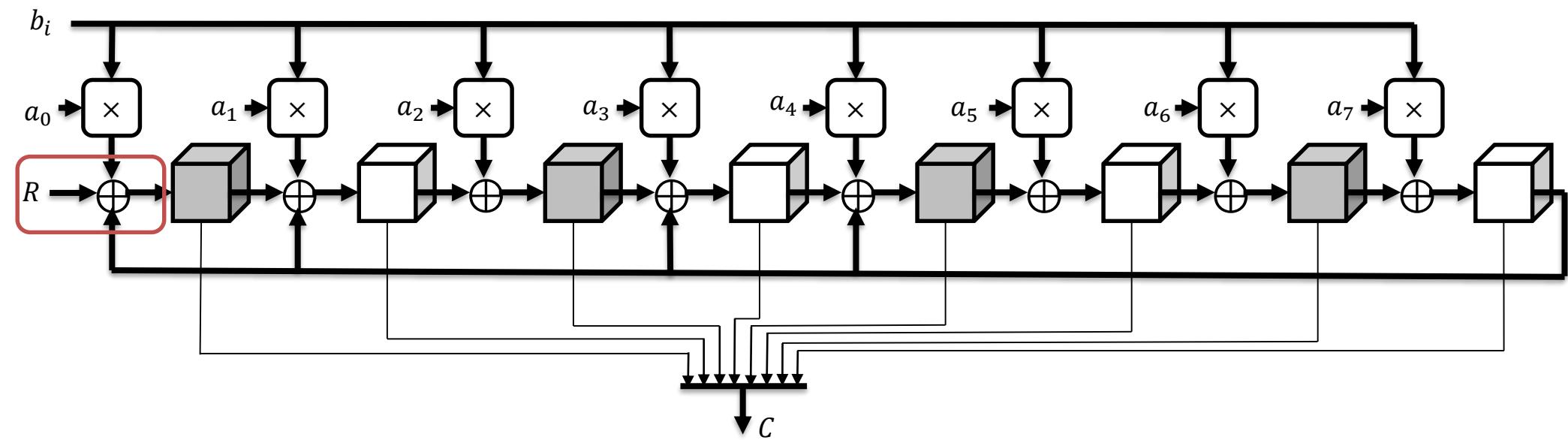
# Serial-Parallel Multiplier

- Inputs:
  - $a$ : 8 bits parallel
  - $b$ : 1 bit serial
- Inject 1 random bit over 8 cycles




# First-order Secure Design (Serial-parallel)

Latency:  
36 cycles

Randomness:  
2 bits / cyc.

Area:  
1378 GE

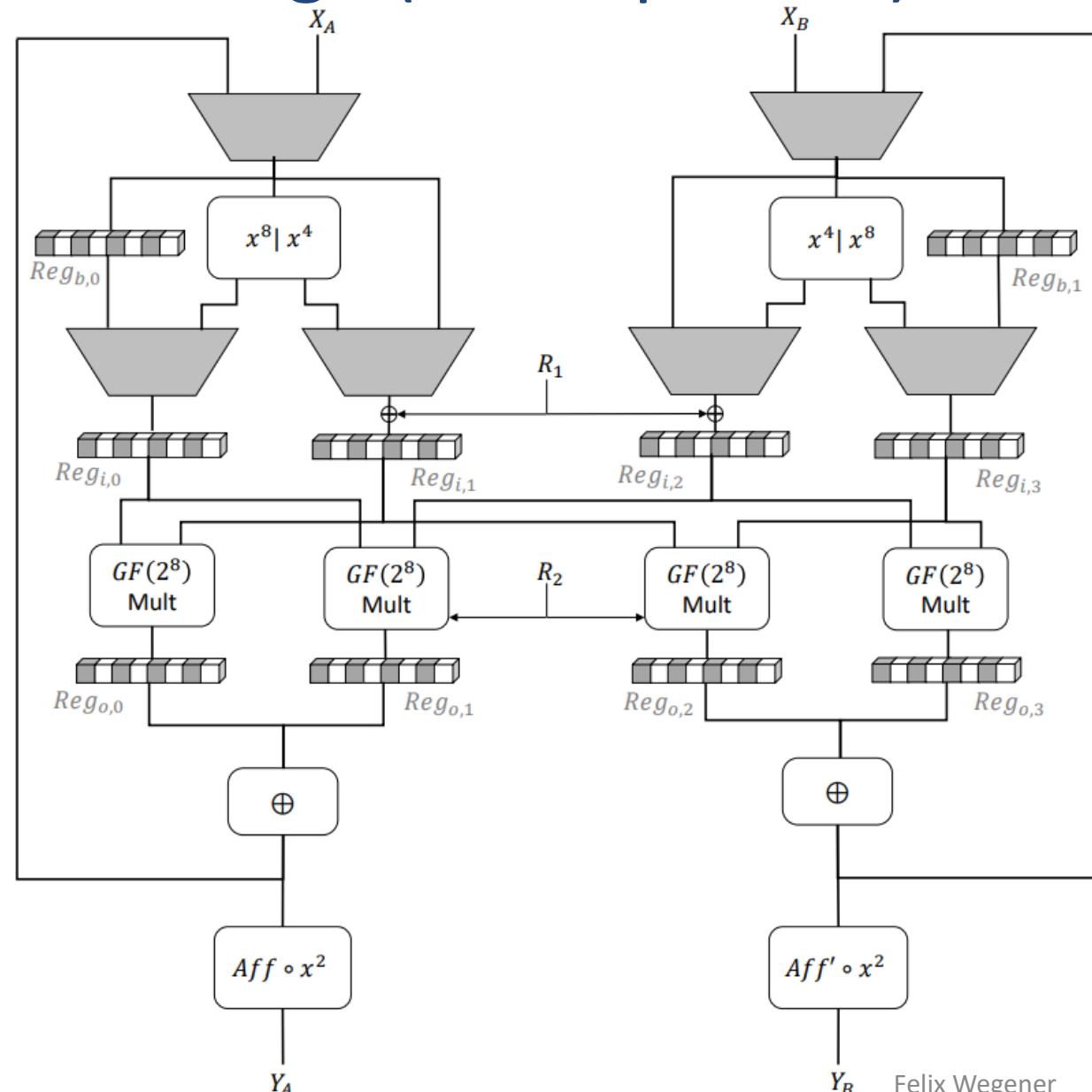


# Side-Channel Evaluation

# SCA Evaluation: Method and Setup

- MC-DPA evaluation
- Sequential execution of S-box
  - First: Derive Power Model
  - Second: CPA

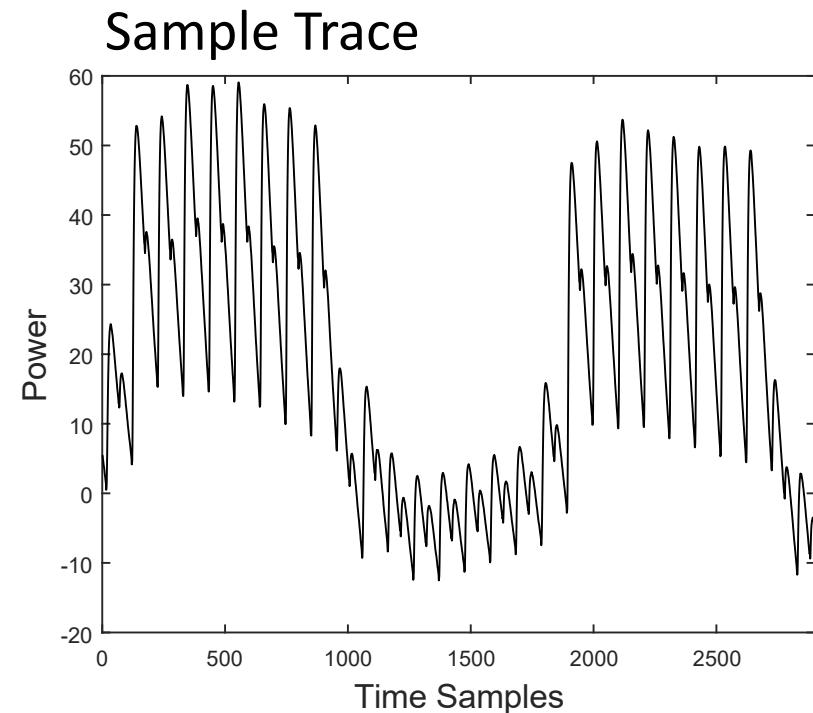
## Setup:

- Sakura-G board @ 6Mhz
- Picoscope 6000 @ 625 MS/s
- No. traces: 10 million




# SCA Evaluation: Results


Serial Design

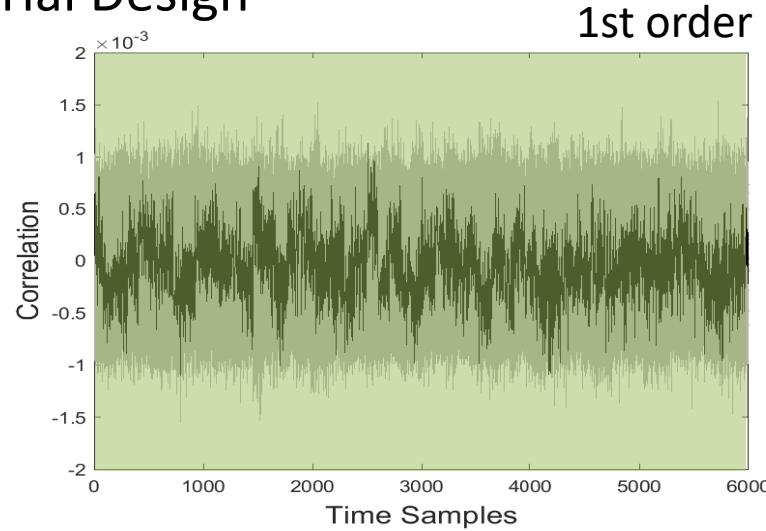


Parallel Design

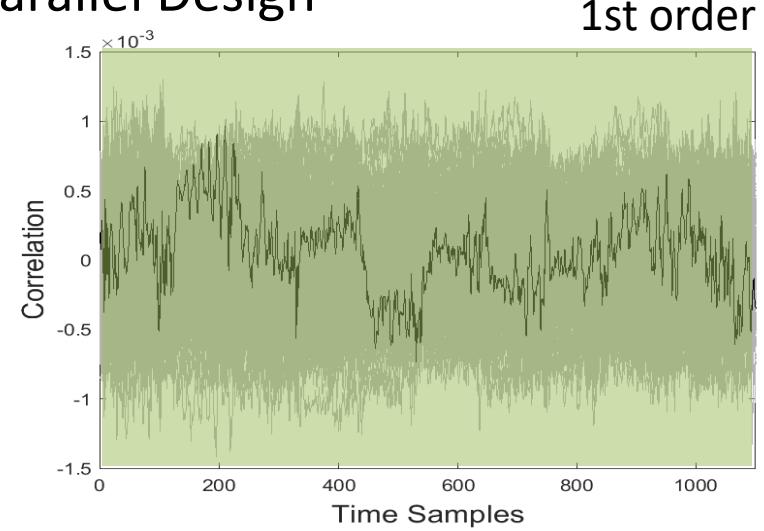

2nd order

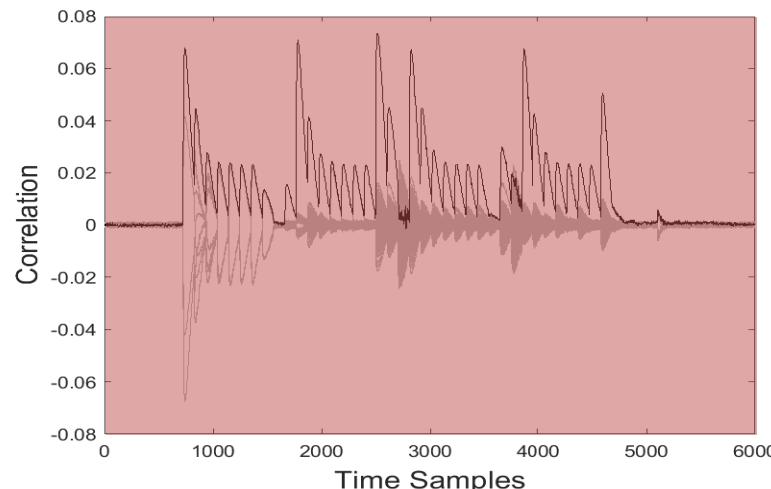

2nd order

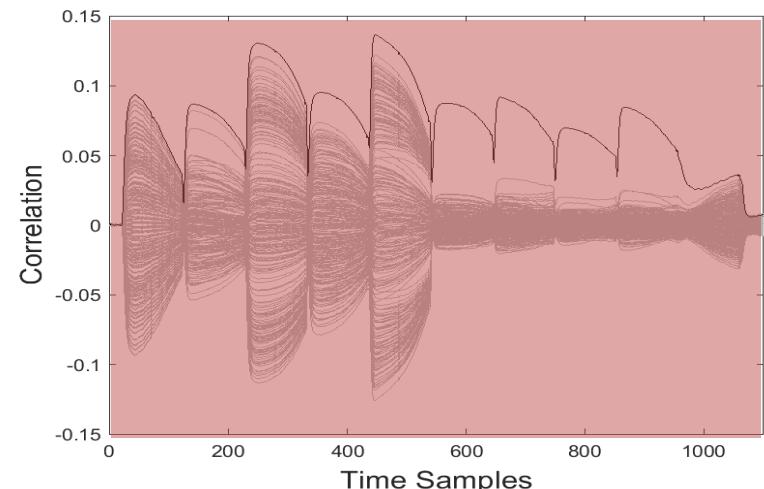

# Comparison: Unprotected Designs

Design	Latency (cycles)	Crit. Path (ns)	Size (GE)
Boyar et al.	1	5.6	205
Serial Design (unprotected)	32	1.5	520

# Comparison: Protected Designs

Design	Shares	Latency (cycles)	Crit. Path (ns)	Rand/Cyc (bits)	Size (GE)
Bilgin et al.	3	3	N/A	16	2224
Cnudde et al.	2	6	N/A	46	1872
Groß et al.	2	8	N/A	18	2600
Ueno et al.	2	5	1.5	56	1656
Former Work	4	16	3.3	0	4200
<b>Parallel Design</b>	<b>2</b>	<b>8</b>	<b>1.6</b>	<b>8</b>	<b>2321</b>
<b>Serial Design</b>	<b>2</b>	<b>36</b>	<b>1.5</b>	<b>2</b>	<b>1378</b>

# Summary

- New first-order secure AES S-box designs:
  - Parallel Design: Interesting trade-off
  - Serial Design:
    - **Smallest** first-order secure AES S-box
    - Only 2 bits of randomness per cycle
- Methodology:

Smallest unprotected design



Smallest protected design

Thanks!  
any questions?

[felix.wegener@rub.de](mailto:felix.wegener@rub.de)

Ruhr University Bochum, Horst Görtz Institute for IT-Security, Germany